

Lec15 Impedance Matching and Tuning (II)

阻抗匹配和调谐


Series Stubs (串行短截线)

EXAMPLE 5.3 SINGLE-STUB SERIES TUNING

Match a load impedance of $Z_L = 100 + j80$ to a 50ohm line using a single series open-circuit stub. Assuming that the load is matched at 2 GHz and that the load consists of a resistor and inductor in series, plot the reflection coefficient magnitude from 1 to 3 GHz.

Smith chart Solution

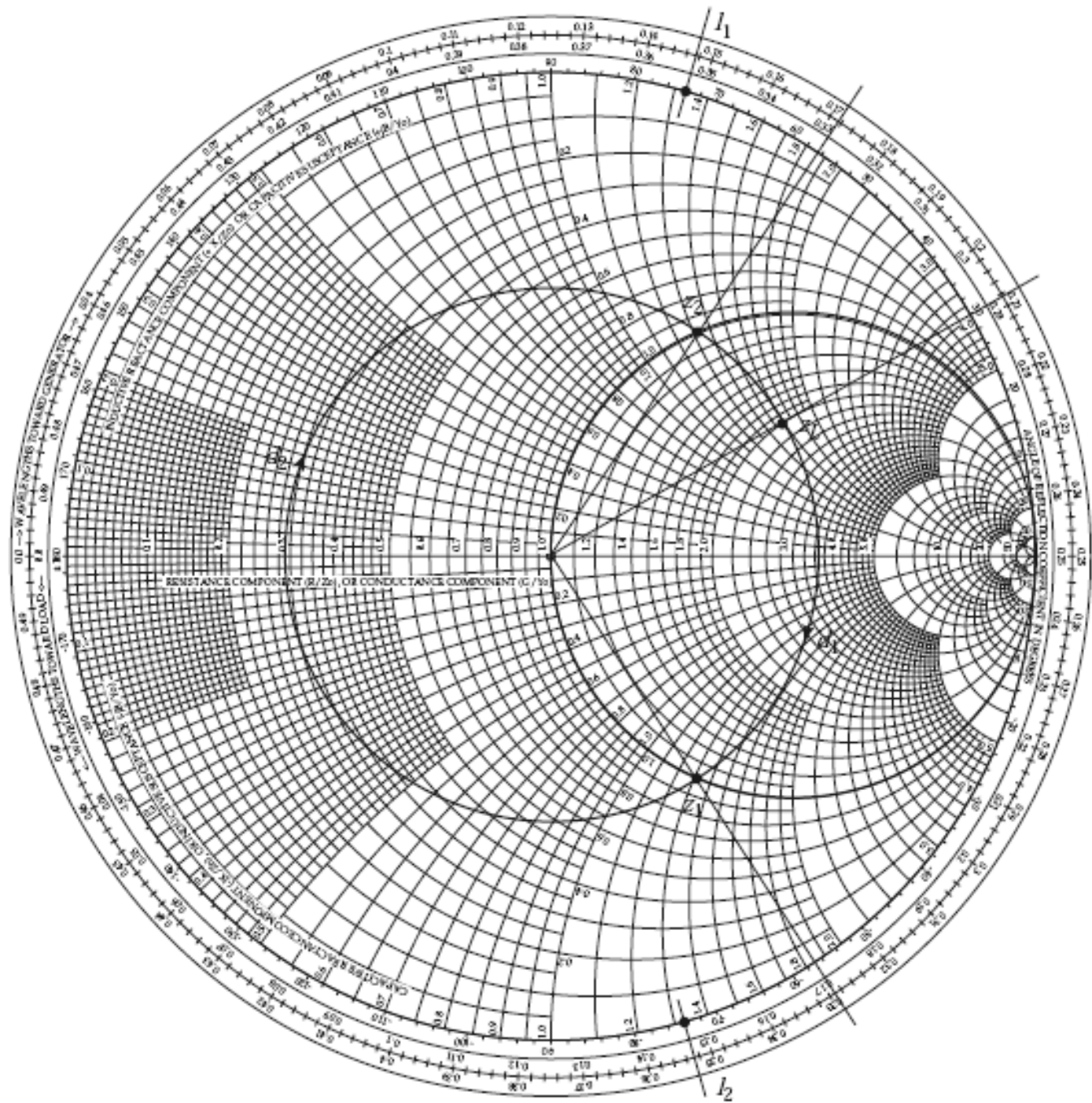- 1) First plot the normalized load impedance, $z_L = 2 + j1.6$, and draw the SWR circle.
- 2) The SWR circle intersects the $1 + jx$ circle at two points, denoted as z_1 and z_2 .



3) The shortest distance, d_1 , from the load to the stub is, from the WTG scale,

$$d_1 = 0.328 - 0.208 = 0.120\lambda,$$

and the second distance is

$$d_2 = (0.5 - 0.208) + 0.172 = 0.463\lambda.$$

The normalized impedances at the two intersection points are

$$z_1 = 1 - j1.33,$$

$$z_2 = 1 + j1.33.$$

4) the first solution requires a stub with a reactance of $j1.33$.

The length of **an open-circuited stub** that gives this reactance can be found on the Smith chart by starting at $z = \infty$ (open circuit), and moving along the outer edge of the chart ($r = 0$) toward the generator to the $j1.33$ point. This gives a stub length of

$$\ell_1 = 0.397\lambda.$$

the required open-circuited stub length for the second solution is

$$\ell_2 = 0.103\lambda.$$

If the load is a series resistor and inductor with $Z_L = 100 + j80$ at 2 GHz, then $R = 100$ and $L = 6.37$ nH. The two matching circuits are shown in the following figure.




Analytical solution

let the load admittance be written as $Y_L = 1/Z_L = G_L + jB_L$.

Then the admittance Y down a length d of line from the load is

$$Y = Y_0 \frac{(G_L + jB_L) + jtY_0}{Y_0 + jt(G_L + jB_L)},$$

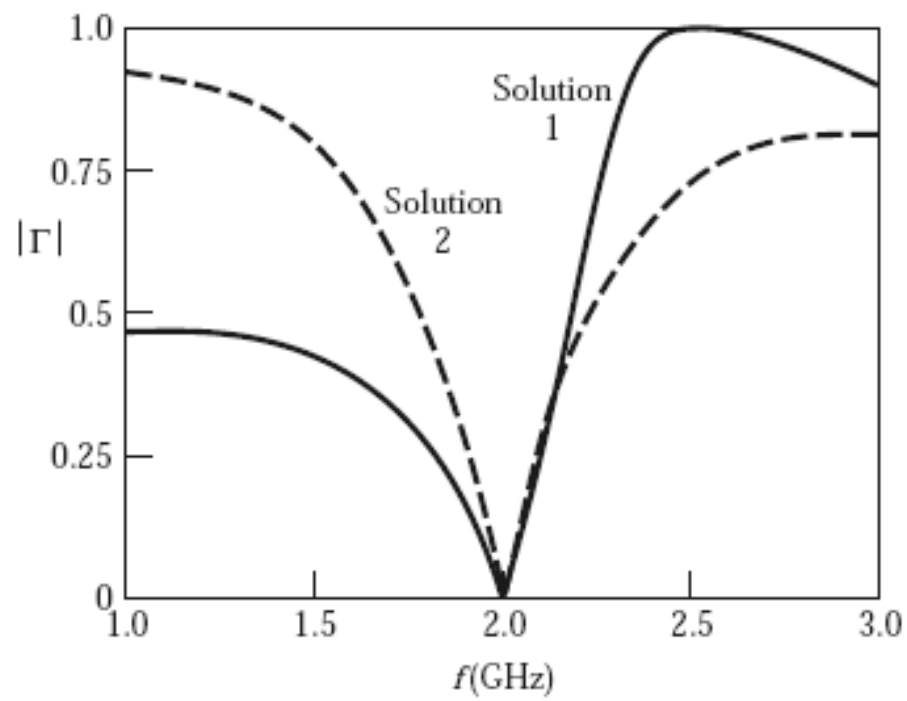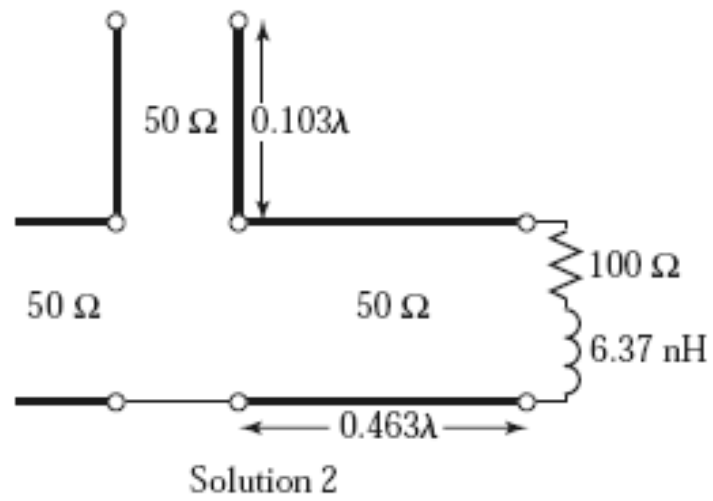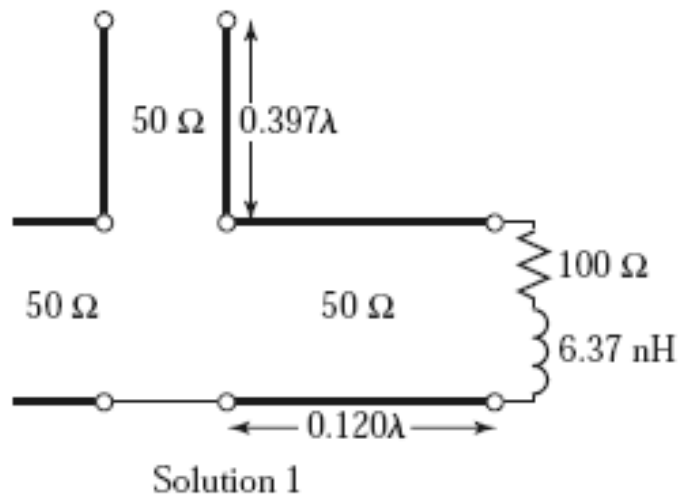where $t = \tan \beta d$ and $Y_0 = 1/Z_0$.



(c)

The impedance at this point is

$$Z = R + jX = \frac{1}{Y},$$

where

$$R = \frac{G_L(1 + t^2)}{G_L^2 + (B_L + Y_0t)^2},$$

$$X = \frac{G_L^2t - (Y_0 - tB_L)(B_L + tY_0)}{Y_0[G_L^2 + (B_L + Y_0t)^2]}.$$

Now d (which implies t) is chosen so that $R = Z_0 = 1/Y_0$.

$$Y_0(G_L - Y_0)t^2 - 2B_L Y_0t + (G_L Y_0 - G_L^2 - B_L^2) = 0.$$

Solving for t gives

$$t = \frac{B_L \pm \sqrt{G_L [(Y_0 - G_L)^2 + B_L^2] / Y_0}}{G_L - Y_0} \quad \text{for } G_L \neq Y_0.$$

If $G_L = Y_0$, then $t = -B_L/2Y_0$.

$$d/\lambda = \begin{cases} \frac{1}{2\pi} \tan^{-1} t & \text{for } t \geq 0 \\ \frac{1}{2\pi} (\pi + \tan^{-1} t) & \text{for } t < 0. \end{cases}$$

The required stub lengths are determined by first using t to find the reactance X . This reactance is the negative of the necessary stub reactance, X_s .

Thus, for a short circuited stub,

$$\frac{\ell_s}{\lambda} = \frac{1}{2\pi} \tan^{-1} \left(\frac{X_s}{Z_0} \right) = \frac{-1}{2\pi} \tan^{-1} \left(\frac{X}{Z_0} \right),$$

and for an open-circuited stub,


$$\frac{\ell_o}{\lambda} = \frac{-1}{2\pi} \tan^{-1} \left(\frac{Z_0}{X_s} \right) = \frac{1}{2\pi} \tan^{-1} \left(\frac{Z_0}{X} \right).$$

If the length given is negative, $\lambda/2$ can be added to give a positive result.

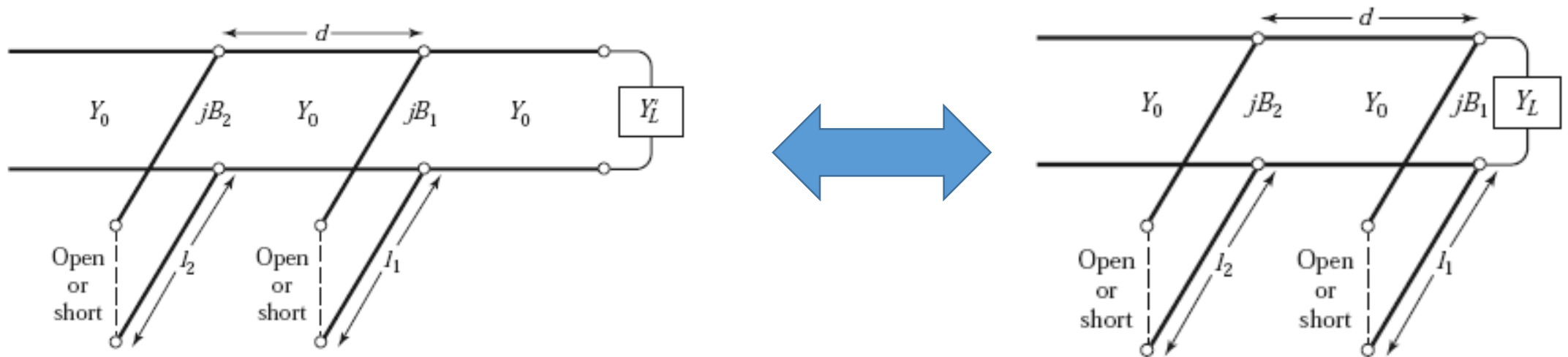
5.3 DOUBLE-STUB TUNING (双短截线调谐)

The **single-stub tuner** is able to match any load impedance (having a positive real part) to a transmission line, but suffers from the disadvantage of requiring a **variable length of line** between the load and the stub.

The **double-stub tuner** uses two tuning stubs in fixed positions.



Smith Chart Solution

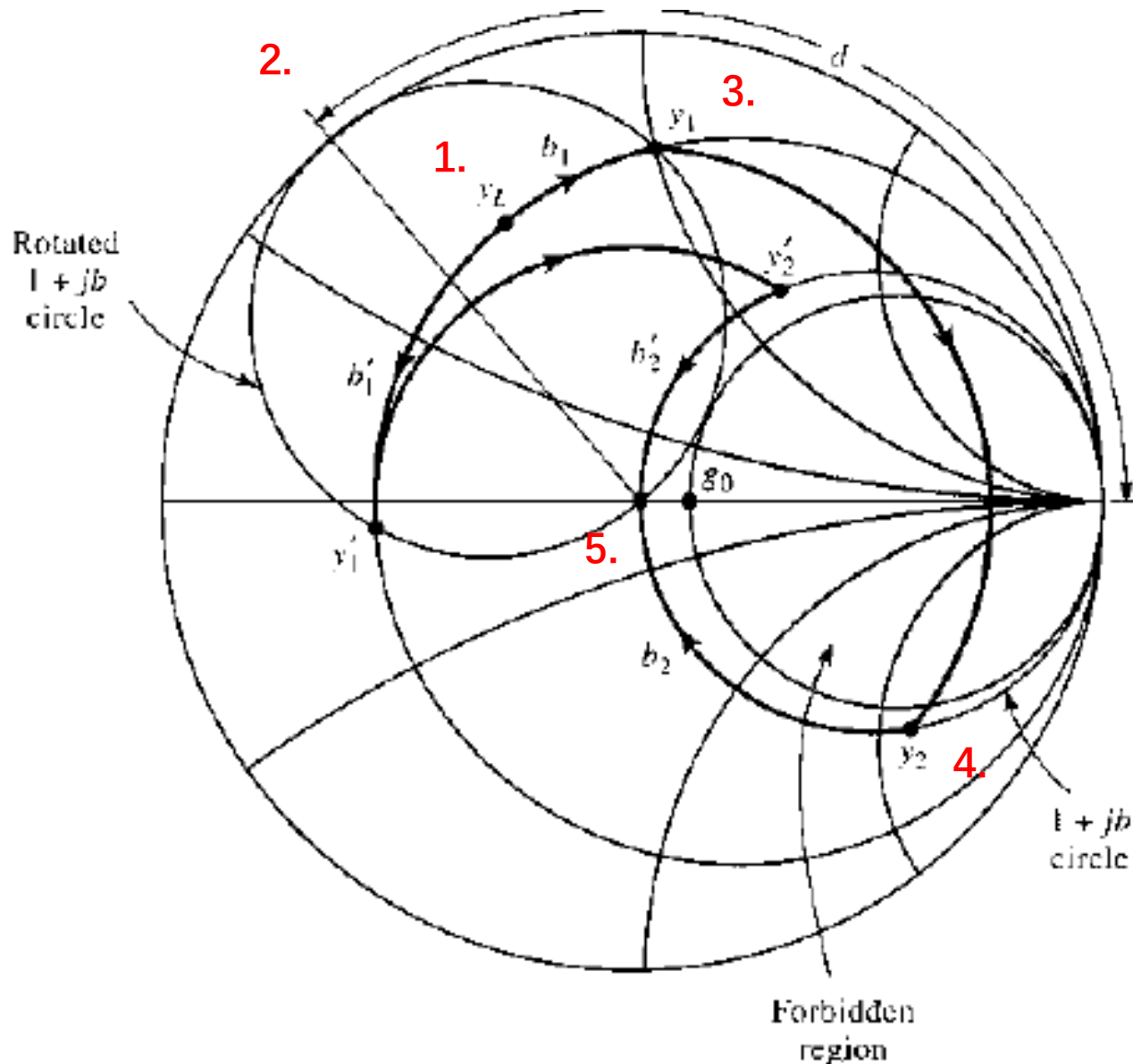

1) Find y_L

2) Rotate $1 + jb$ circle, the amount of rotation is d wavelengths toward the load.

3) move the load admittance to y_1 and y_1' .

4) Move y_1 to y_2 ; move y_1' to y_2' .


5) Move y_2 and y_2' to the center of smith chart.

The forbidden area is inside the shaded region of the $g_0 + jb$ circle, no value of stub susceptance b_1 could ever bring the load point to intersect the rotated $1 + jb$ circle.

A simple way of **reducing the forbidden range** is to **reduce the distance d** between the stubs. This has the effect of swinging the rotated $1 + jb$ circle back toward the $y = \infty$ point, but d must be kept large enough for the practical purpose of fabricating the two separate stubs. In addition, **stub spacings near 0 or $\lambda/2$ lead to matching networks that are very frequency sensitive**. In practice, stub spacings are usually chosen as **$\lambda/8$ or $3\lambda/8$** .

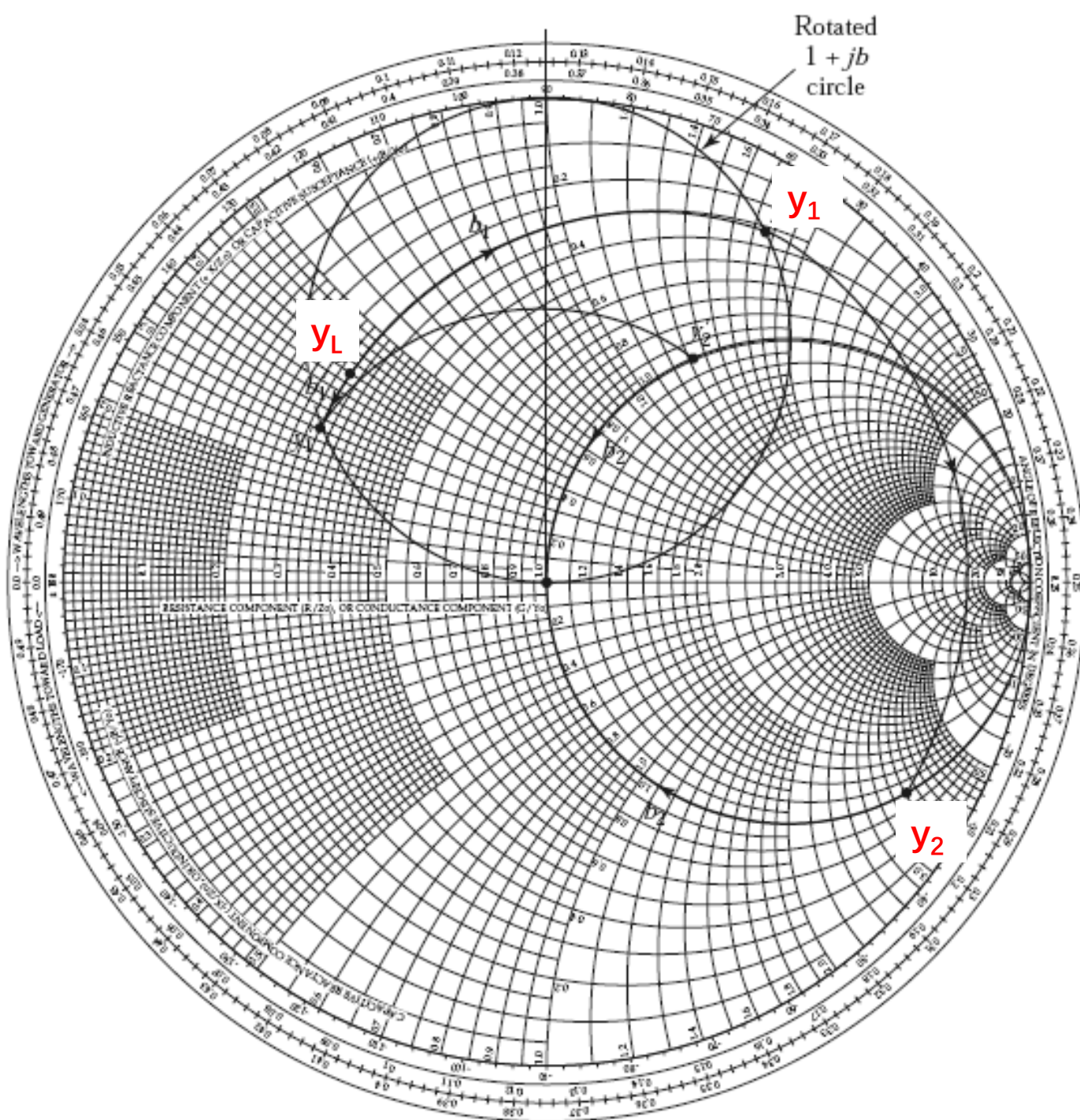EXAMPLE 5.4 DOUBLE-STUB TUNING

Design a double-stub shunt tuner to match a load impedance $Z_L = 60 - j80$ to a $50 \text{ } \Omega$ line. *The stubs are to be open-circuited stubs and are spaced $\lambda/8$ apart.* Assuming that this load consists of a series resistor and capacitor and that the match frequency is 2 GHz, plot the reflection coefficient magnitude versus frequency from 1 to 3 GHz.



1) $y_L = 0.3 + j0.4$.

2) move y_L to y_1 and y_1' and then

$$b_1 = 1.314 \quad \text{or} \quad b_1' = -0.114.$$

3) transform through the $\lambda/8$ section of line by rotating along a constant radius (SWR) circle $\lambda/8$ toward the generator.

$$y_2 = 1 - j3.38 \quad \text{or} \quad y_2' = 1 + j1.38.$$

4) Then the susceptance of the second stub should be


$$b_2 = 3.38 \quad \text{or} \quad b_2' = -1.38.$$


The lengths of the open-circuited stubs are then found as

$$\ell_1 = 0.146\lambda, \ell_2 = 0.204\lambda \quad \text{or} \quad \ell'_1 = 0.482\lambda, \ell'_2 = 0.350\lambda.$$

This completes both solutions for the double-stub tuner design.

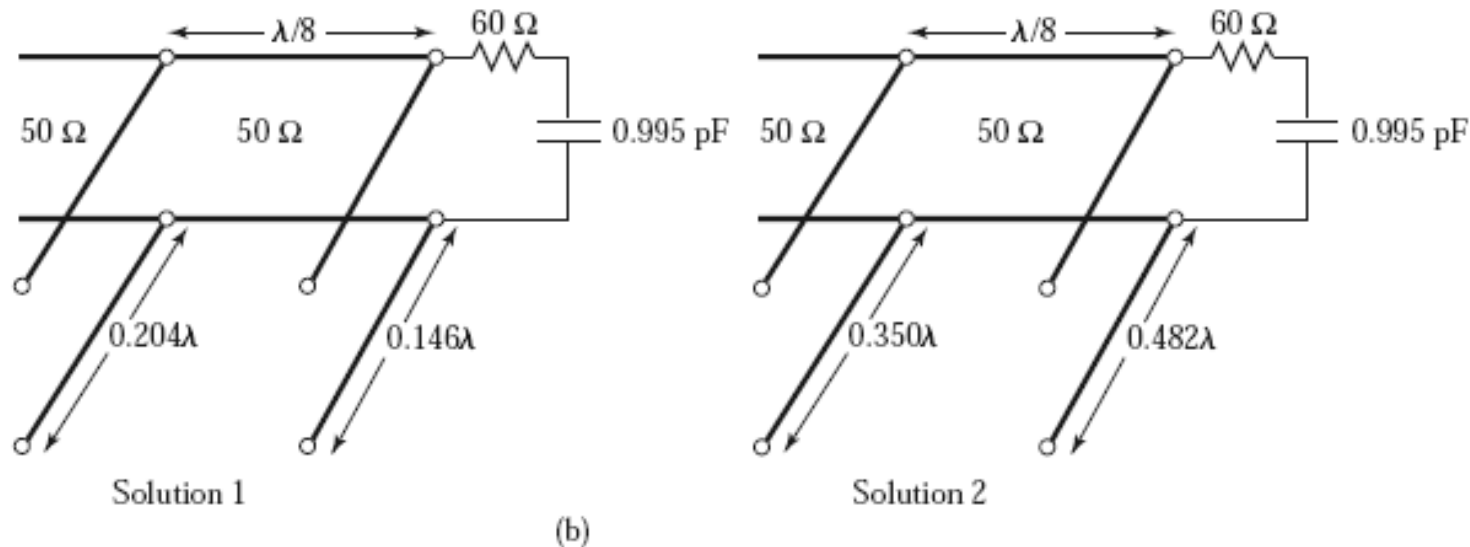At $f = 2$ GHz the resistor-capacitor load of $Z_L = 60 - j80$ implies that $R = 60$ and $C = 0.995$ pF.



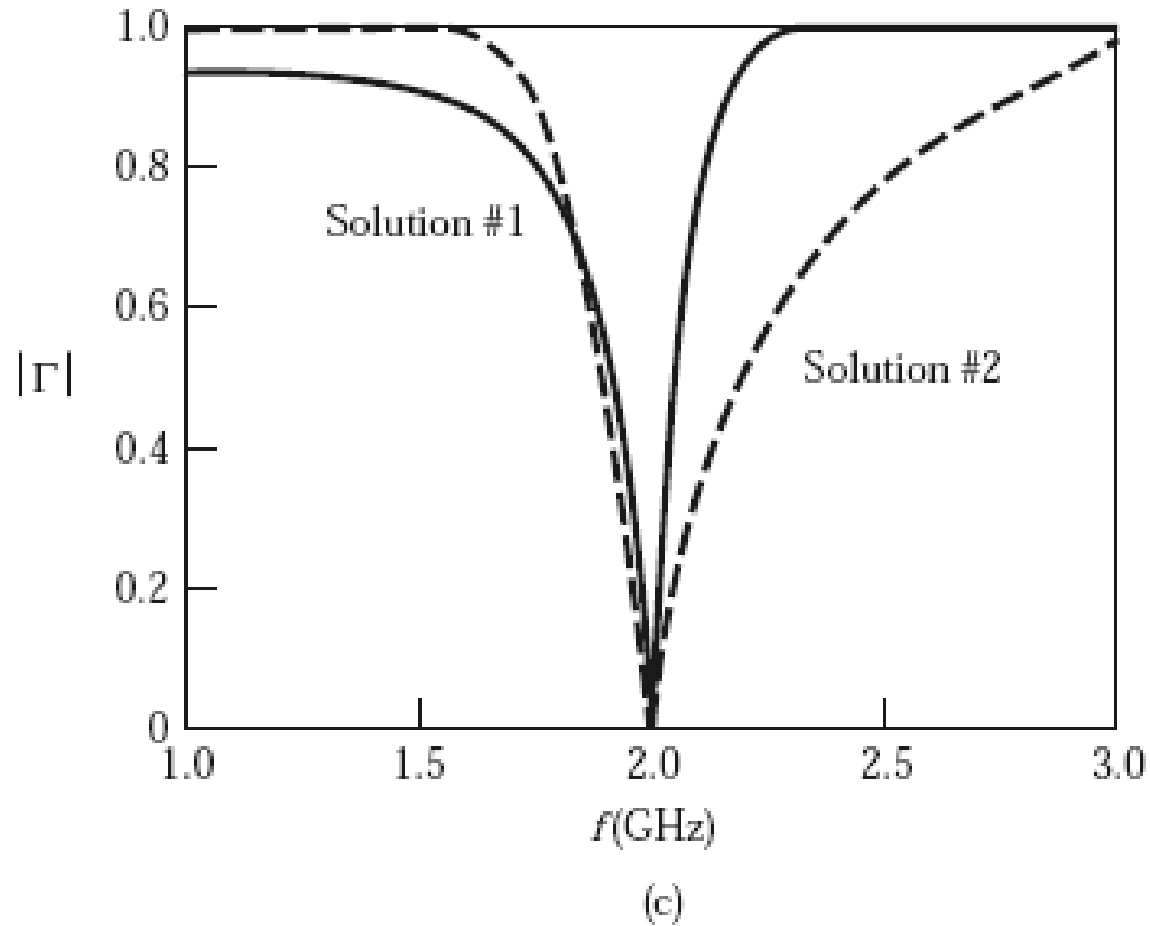

Note that the first solution has a much narrower bandwidth than the second (primed) solution due to the fact that both stubs for the first solution are somewhat longer (and **closer to $\lambda/2$**) than the stubs of the second solution.

Analytic Solution

The admittance just to the left of the first stub is

$$Y_1 = G_L + j(B_L + B_1),$$

where $Y_L = G_L + j B_L$ is the load admittance, and B_1 is the susceptance of the first stub.

After transforming through a length d of transmission line, we find that the admittance just to the right of the second stub is

$$Y_2 = Y_0 \frac{G_L + j(B_L + B_1 + Y_0 t)}{Y_0 + jt(G_L + jB_L + jB_1)},$$

where $t = \tan \beta d$ and $Y_0 = 1/Z_0$.

At this point the real part of Y_2 must equal Y_0 ,

$$G_L^2 - G_L Y_0 \frac{1 + t^2}{t^2} + \frac{(Y_0 - B_L t - B_1 t)^2}{t^2} = 0.$$

Solving for GL gives

$$G_L = Y_0 \frac{1+t^2}{2t^2} \left[1 \pm \sqrt{1 - \frac{4t^2(Y_0 - B_L t - B_1 t)^2}{Y_0^2(1+t^2)^2}} \right].$$

Because GL is real, the quantity within the square root must be nonnegative, and so

$$0 \leq \frac{4t^2(Y_0 - B_L t - B_1 t)^2}{Y_0^2(1+t^2)^2} \leq 1.$$

This implies that

$$0 \leq G_L \leq Y_0 \frac{1+t^2}{t^2} = \frac{Y_0}{\sin^2 \beta d},$$

which gives **the range on GL** that can be matched for a given stub spacing d .

After d has been set, the first stub susceptance can be determined as

$$B_1 = -B_L + \frac{Y_0 \pm \sqrt{(1+t^2)G_L Y_0 - G_L^2 t^2}}{t}.$$

Then the second stub susceptance can be found from the negative of the imaginary part of Y_2

$$B_2 = \frac{\pm Y_0 \sqrt{Y_0 G_L (1 + t^2) - G_L^2 t^2} + G_L Y_0}{G_L t}.$$

The open-circuited stub length is found as

$$\frac{\ell_o}{\lambda} = \frac{1}{2\pi} \tan^{-1} \left(\frac{B}{Y_0} \right),$$

and the short-circuited stub length is found as

$$\frac{\ell_s}{\lambda} = \frac{-1}{2\pi} \tan^{-1} \left(\frac{Y_0}{B} \right),$$

where $B = B_1$ or B_2 .

Homework

- 5.9 Design a double-stub tuner using open-circuited stubs with a $\lambda/8$ spacing to match a load admittance $Y_L = (0.4 + j1.2)Y_0$.