




上海交通大学  
SHANGHAI JIAO TONG UNIVERSITY



# Lecture 15

## MOSFET Equivalent Circuit Models

 




# Outline

**Large-signal model**

**Low-frequency small-signal equivalent circuit model**


 
**High-frequency small-signal equivalent circuit model**





# Large Signal Model for NMOS Transistor

- Regimes of operation:

 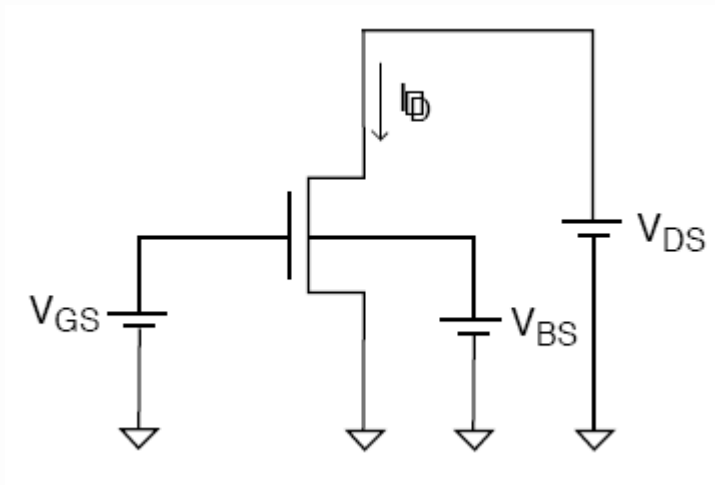



- **Cut-off**

$$I_D = 0$$

- **Linear / Triode:**

$$I_D = \frac{W}{L} \mu_n \left[ V_{GS} - \frac{V_{DS}}{2} - V_T \right] \cdot V_{DS}$$

- **Saturation Regimes of operation:**

$$I_D = I_{Dsat} = \frac{W}{2L} \mu_n C_{ox} [V_{GS} - V_T]^2 \cdot [1 + \lambda V_{DS}]$$



- **Effect of back bias**

$$V_T(V_{BS}) = V_{To} + \gamma \left[ \sqrt{-2\phi_p - V_{BS}} - \sqrt{-2\phi_p} \right]$$


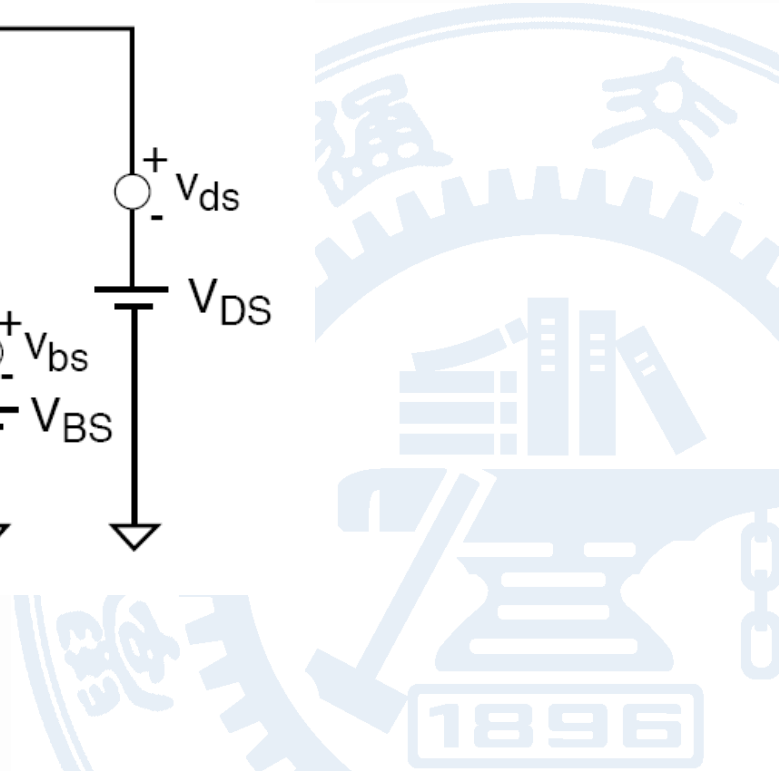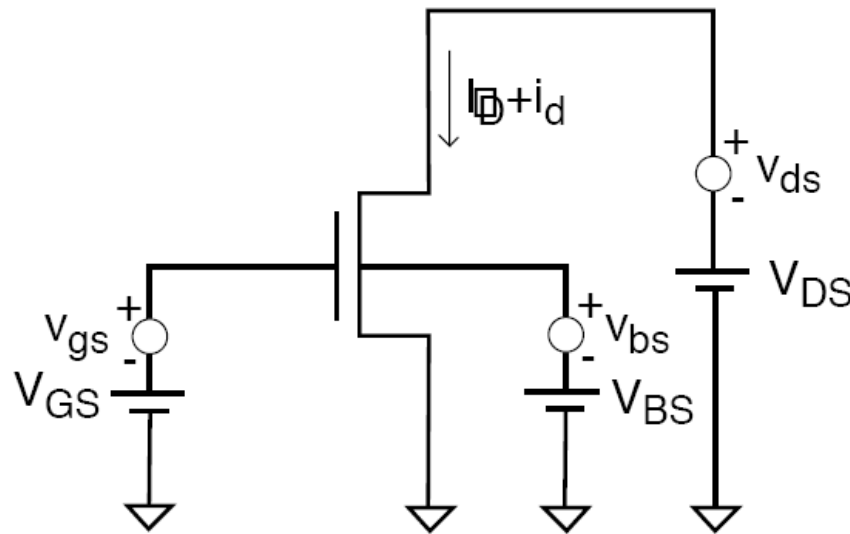
# Small-signal device modeling

In many applications, we are only interested in the response of the device to a small-signal applied on top of a bias.





## Key Points:

- Small-signal is small
  - response of non-linear components becomes linear
- Since response is linear, lots of linear circuit techniques such as superposition can be used to determine the circuit response.
- Notation:  $i_D = I_D + i_d$  --- Total = DC + Small Signal

Mathematically:

$$i_D (V_{GS}, V_{DS}, V_{BS}; v_{gs}, v_{ds}, v_{bs}) \approx I_D (V_{GS}, V_{DS}, V_{BS}) + i_d (v_{gs}, v_{ds}, v_{bs})$$



With  $i_d$  linear on small-signal drives:

$$i_d = g_m v_{gs} + g_o v_{ds} + g_{mb} v_{bs}$$

Define  $g_m$  transconductance [S]

$g_o$  output or drain conductance [S]

$g_{mb}$  backgate transconductance [S]

Approach to computing  $g_m$ ,  $g_o$ , and  $g_{mb}$ .

$$g_m \approx \left. \frac{\partial i_D}{\partial v_{GS}} \right|_Q$$

$$g_o \approx \left. \frac{\partial i_D}{\partial v_{DS}} \right|_Q$$

$$g_{mb} \approx \left. \frac{\partial i_D}{\partial v_{BS}} \right|_Q$$

$$Q = [v_{GS} = V_{GS}, v_{DS} = V_{DS}, v_{BS} = V_{BS}]$$



# Transconductance

In saturation regime:


$$i_D = \frac{W}{2L} \mu_n C_{ox} [v_{GS} - V_T]^2 \cdot [1 + \lambda V_{DS}]$$

Then (neglecting channel length modulation)  
the transconductance is:



$$g_m = \left. \frac{\partial i_D}{\partial v_{GS}} \right|_Q \approx \frac{W}{L} \mu_n C_{ox} (V_{GS} - V_T)$$

Rewrite in terms of  $I_D$ :
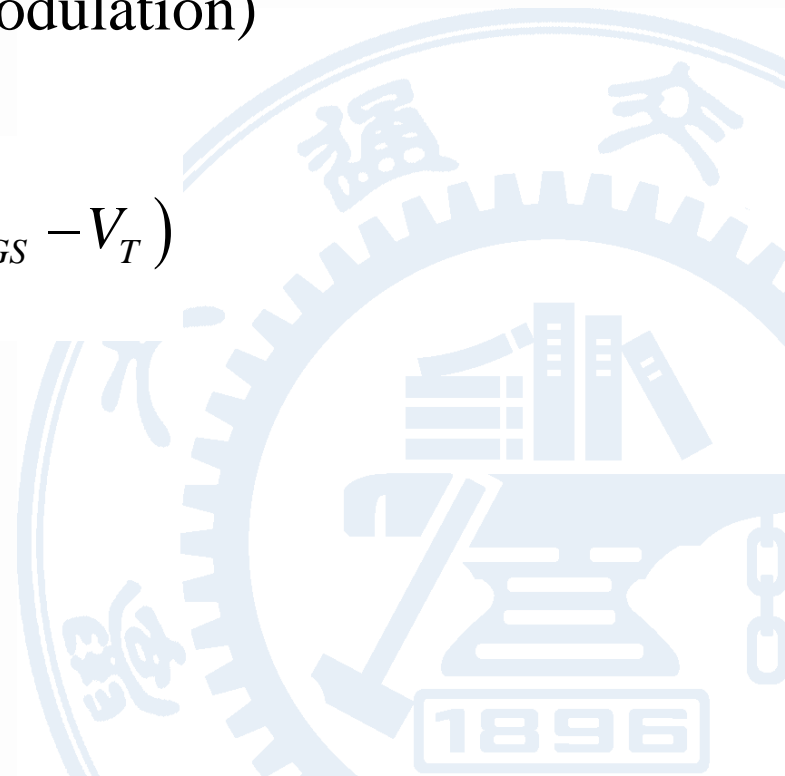
$$g_m = \sqrt{2 \frac{W}{L} \mu_n C_{ox} I_D}$$








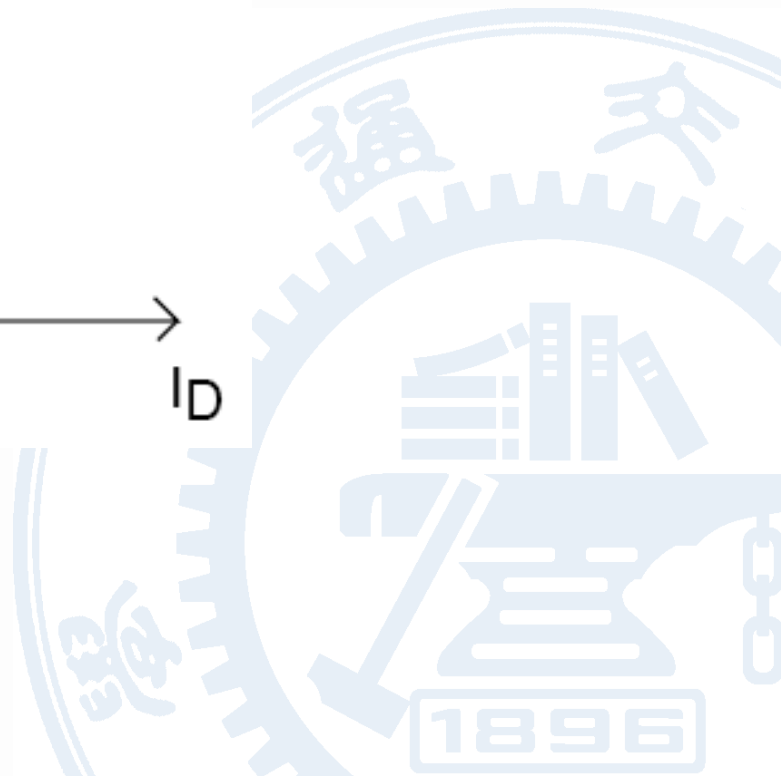 


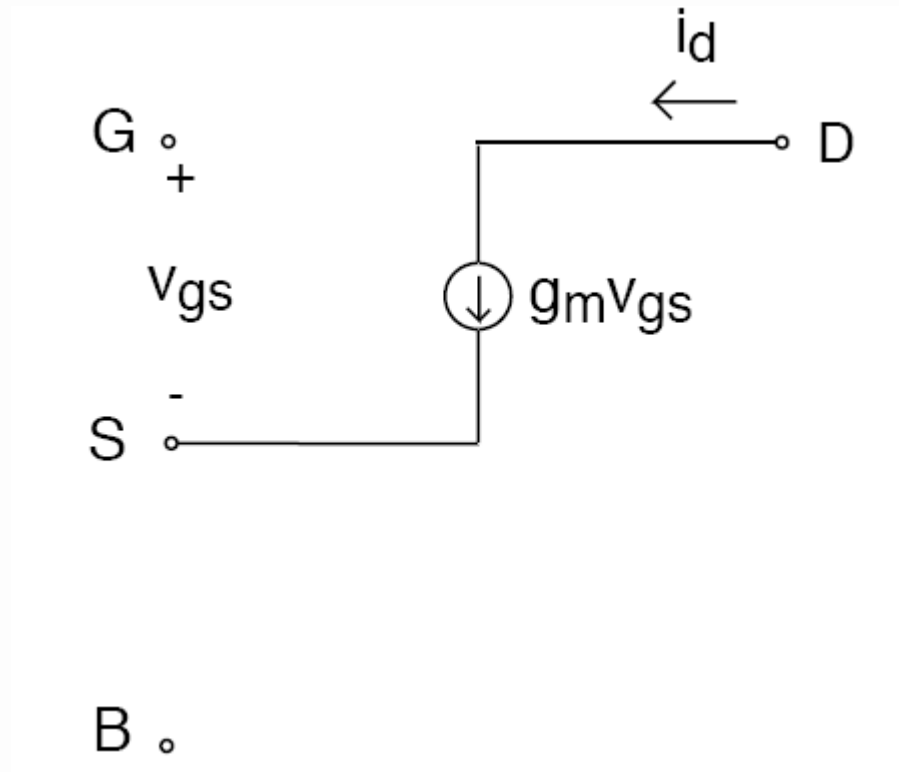
## Equivalent circuit model representation of $g_m$ :



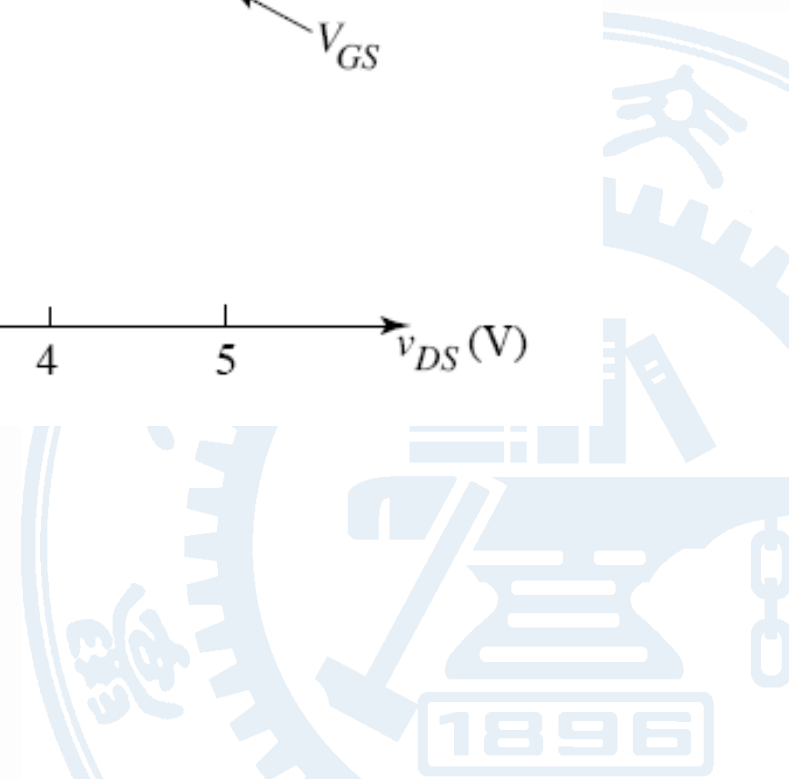 



# Output conductance

In saturation regime:


$$i_D = \frac{W}{2L} \mu_n C_{ox} [v_{GS} - V_T]^2 \cdot [1 + \lambda v_{DS}]$$

Then:

$$g_0 = \left. \frac{\partial i_D}{\partial v_{DS}} \right|_Q = \frac{W}{2L} \mu_n C_{ox} (V_{GS} - V_T)^2 \cdot \lambda \approx \lambda I_D$$

Output resistance is the inverse of output conductance:
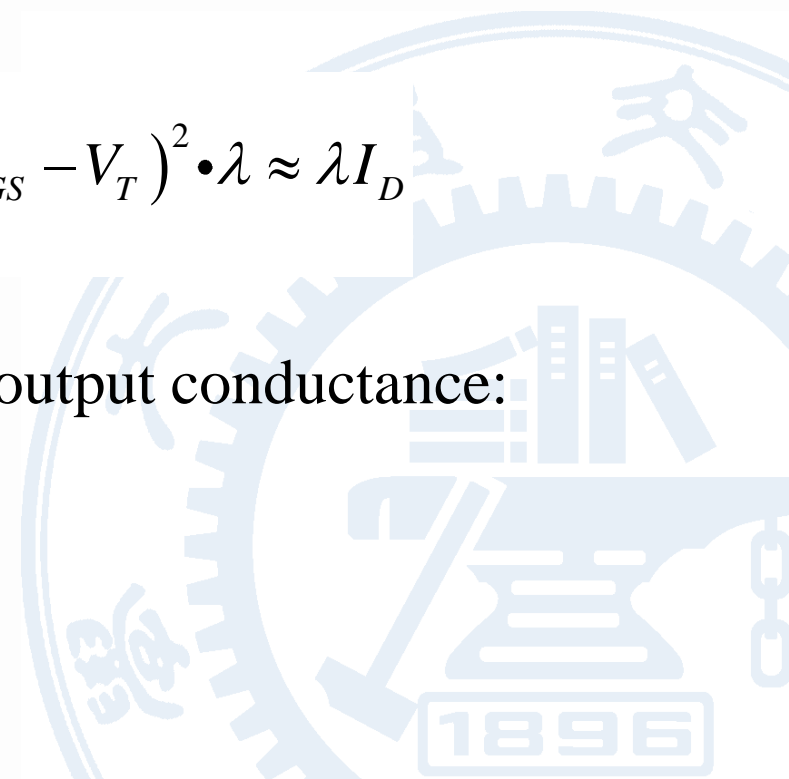
$$r_0 = \frac{1}{g_0} = \frac{1}{\lambda I_D}$$








Remember also:  $\lambda \propto \frac{1}{L}$

Hence:  $r_o \propto L$

  Equivalent circuit model representation of  $g_o$ :



 



## Backgate transconductance

In saturation regime (neglect channel length modulation):

$$i_D \approx \frac{W}{2L} \mu_n C_{ox} [v_{GS} - V_T]^2$$

Then

$$g_{mb} = \left. \frac{\partial i_D}{\partial v_{BS}} \right|_Q = -\frac{W}{L} \mu_n C_{ox} (V_{GS} - V_T) \cdot \left( \left. \frac{\partial V_T}{\partial v_{BS}} \right|_Q \right)$$

Since

$$V_T(v_{BS}) = V_{T_0} + \gamma \left[ \sqrt{-2\phi_p - v_{BS}} - \sqrt{-2\phi_p} \right]$$


$$\left. \frac{\partial V_T}{\partial v_{BS}} \right|_Q = \frac{-\gamma}{2\sqrt{-2\phi_p - V_{BS}}}$$




Hence:

$$g_{mb} = \frac{\gamma g_m}{2\sqrt{-2\phi_p - V_{BS}}}$$

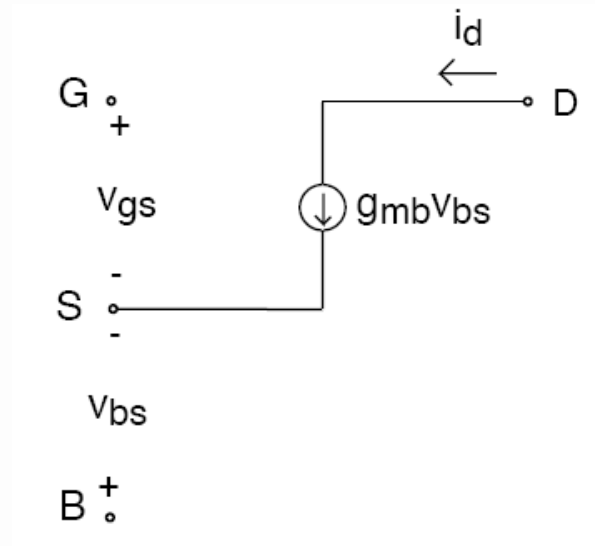Equivalent circuit representation of  $g_{mb}$ :






 


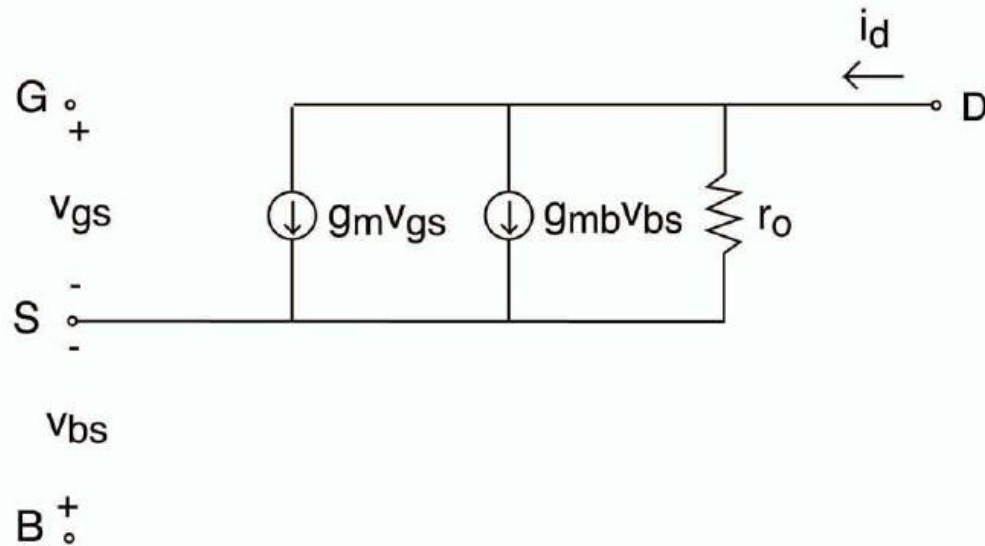
# Complete MOSFET small-signal Equivalent circuit model for low frequency:






# High-frequency small-signal equivalent circuit model

Need to add capacitances and resistance.

In saturation:

 




$C_{gs}$  = channel charge + overlap capacitance  $C_{ov}$ ,

$C_{gd}$  = overlap capacitance,  $C_{ov}$ ,

$C_{sb}$  = source junction depletion capacitance (+sidewall)

$C_{db}$  = drain junction depletion capacitance (+sidewall)

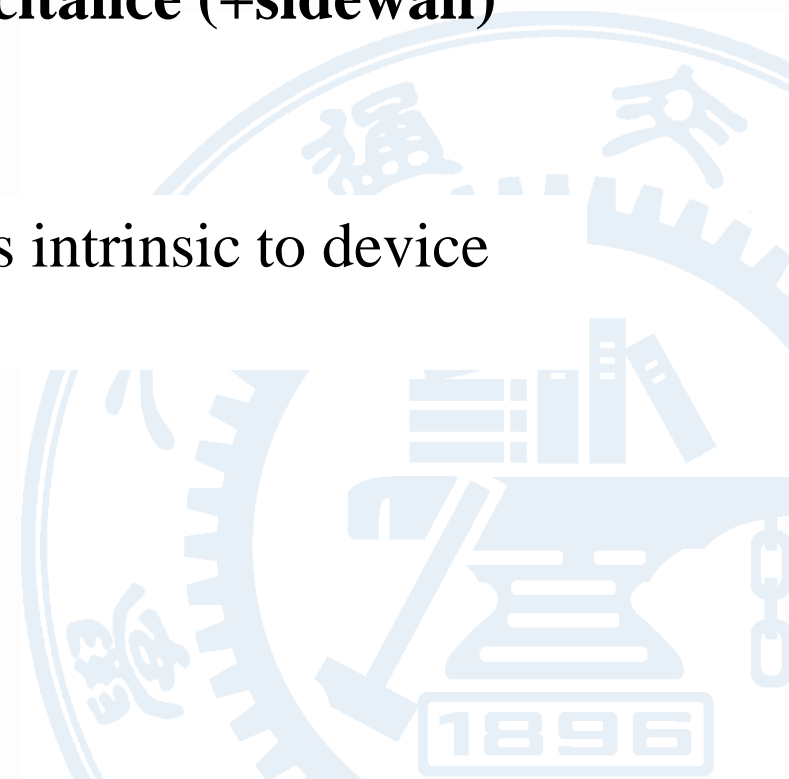ONLY Channel Charge Capacitance is intrinsic to device operation. All others are parasitic.





## Inversion layer charge in saturation

$$q_N(v_{GS}) = W \int_0^L Q_N(y) dy = W \int_0^{v_{GS} - V_T} Q_N(v_C) \cdot \frac{dy}{dv_C} \cdot dv_C$$

Note that  $q_N$  is total inversion charge in the channel &  $v_C(y)$  is the channel voltage. But:

$$\frac{dv_C}{dy} = - \frac{i_D}{W \mu_n Q_N(v_C)}$$



$$I_D = -W \cdot Q_N(y) \cdot v_y(y)$$

$$v_y(y) = -\mu_n \cdot E_y(y) = \mu_n \cdot \frac{dV}{dy}$$

Then:

$$q_N(v_{GS}) = - \frac{W^2 \mu_n}{i_D} \cdot \int_0^{V_{GS} - V_T} [Q_N(v_C)]^2 \cdot dv_C$$



Remember:  $Q_N(v_C) = -C_{ox} [v_{GS} - v_C(y) - V_T]$

Then:

$$q_N(v_{GS}) = -\frac{W^2 \mu_n C_{ox}^2}{i_D} \cdot \int_0^{v_{GS} - V_T} [v_{GS} - v_C(y) - V_T]^2 \cdot dv_C$$

Do integral, substitute  $i_D$  in saturation and get:

$$q_N(v_{GS}) = -\frac{2}{3} WLC_{ox} (v_{GS} - V_T)$$

Gate charge:  $q_G(v_{GS}) = -q_N(v_{GS}) - Q_{B,\max}$

Intrinsic gate-to-source capacitance:

$$C_{gs,i} = \frac{dq_G}{dv_{GS}} = \frac{2}{3} WLC_{ox}$$



Must add overlap capacitance:

$$C_{gs} = \frac{2}{3}WLC_{ox} + WC_{ov}$$


Gate-to-drain capacitance — only overlap capacitance:

$$C_{gd} = WC_{ov}$$





# Other capacitances

 





## Source-to-Bulk capacitance:

$$C_{sb} = WL_{diff} C_j + (2L_{diff} + W)C_{jsw}$$

where  $C_j$ : Bottom Wall at  $V_{SB}$  ( $F / cm^2$ )

$C_{jsw}$ : Side Wall at  $V_{SB}$  ( $F / cm$ )

## Drain-to-Bulk capacitance:


$$C_{db} = WL_{diff} C_j + (2L_{diff} + W)C_{jsw}$$

where  $C_j$ : Bottom Wall at  $V_{DB}$  ( $F / cm^2$ )

$C_{jsw}$ : Side Wall at  $V_{DB}$  ( $F / cm$ )

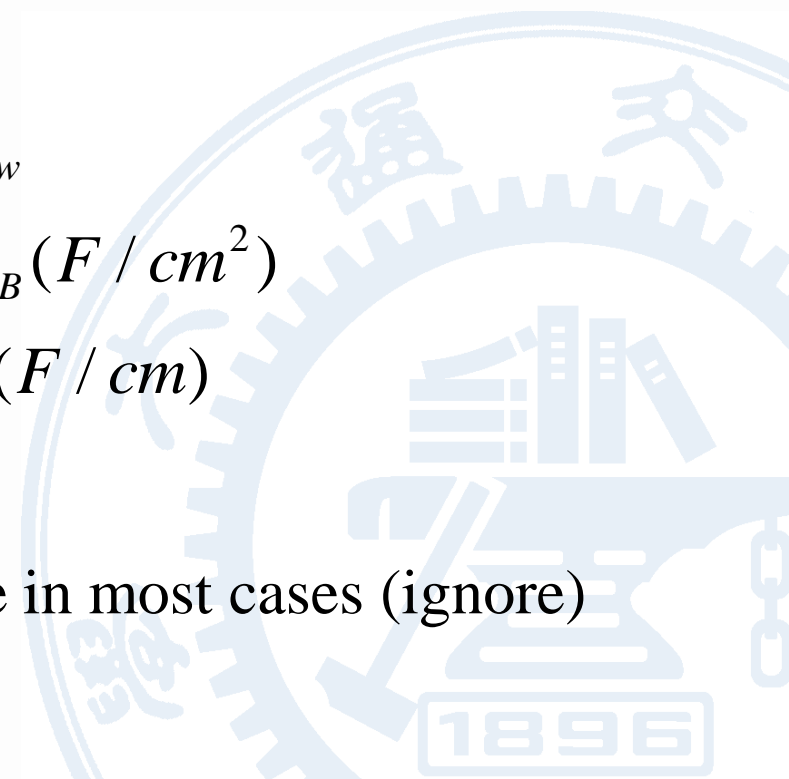
## Gate-to-Bulk capacitance:

$C_{gb} \equiv$  small parasitic capacitance in most cases (ignore)




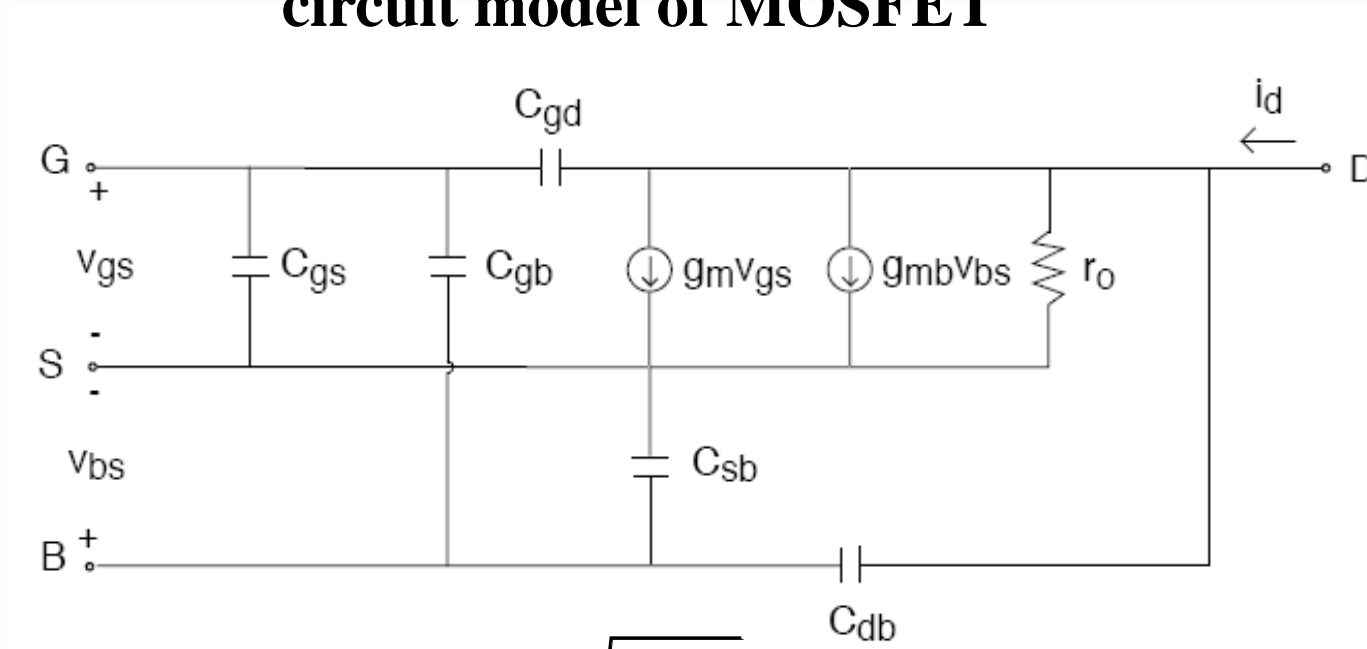
## High-frequency small-signal equivalent circuit model of MOSFET



In saturation:

$$g_m \propto \sqrt{\frac{W}{L}} I_D$$

$$r_o \propto \frac{L}{I_D}$$

$$C_{gs} \propto WLC_{ox}$$





## Frequency Limitation factors and Cutoff Frequency

Two frequency Limitation factors:

- Channel transit time
- Capacitance charging time – dominating factor

### 1. Channel transit time

$$\tau_t = \frac{L}{v}$$

The minimum channel transit time is

$$\tau_{t \min} = \frac{L}{v_{sat}}$$

The maximum frequency is

$$f_{\max} = \frac{1}{\tau_{t \min}}$$





## 2. Capacitance charging time

 


Fig. High frequency small signal model

 


Fig. High frequency small signal equivalent circuit model including miller capacitance

The input current is

$$I_i = j\omega C_{gsT} V_{gs} + j\omega C_{gdT} (V_{gs} - V_d)$$

Summing the output current

$$\frac{V_d}{R_L} + g_m V_{gs} + j\omega C_{gdT} (V_d - V_{gs}) = 0$$

Combining the two equations to eliminate the voltage variable  $V_d$ , then

$$I_i = j\omega \left[ C_{gsT} + C_{gdT} \left( \frac{1 + g_m R_L}{1 + j\omega R_L C_{gdT}} \right) \right] V_{gs}$$

Normally,  $\omega R_L C_{gdT}$  is much less than unity

$$I_i = j\omega [C_{gsT} + C_{gdT} (1 + g_m R_L)] V_{gs}$$

The miller capacitance is then

$$C_M = C_{gdT} (1 + g_m R_L)$$



## •Cutoff frequency

the frequency at which the magnitude of the current gain of the device is unity

$$I_i = j\omega(C_{gsT} + C_M)V_{gs} \quad I_d = g_m V_{gs}$$

$$\left| \frac{I_d}{I_i} \right| = \frac{g_m}{2\pi f(C_{gsT} + C_M)} = 1$$

$$f_T = \frac{g_m}{2\pi(C_{gsT} + C_M)} = \frac{g_m}{2\pi C_G}$$

When the ideal MOSFET is biased in the saturation region,  $C_{gd}$  approaches zero and  $C_{gs}$  is approximately  $C_{ox}WL$ , and the transconductance is

$$g_{ms} = \frac{W\mu_n C_{ox}}{L} (V_{GS} - V_T)$$

The cutoff frequency is

$$f_T = \frac{g_m}{2\pi C_G} = \frac{\frac{W\mu_n C_{ox} (V_{GS} - V_T)}{L}}{2\pi C_{ox} WL} = \frac{\mu_n (V_{GS} - V_T)}{2\pi L^2}$$



## •Source resistance effect

 


Figure Simplified, low frequency small-signal equivalent circuit of common-source n-channel MOSFET including source resistance

$$V_{gs} = V'_{gs} + (g_m V'_{gs}) r_s = (1 + g_m r_s) V'_{gs}$$

$$I_d = \left( \frac{g_m}{1 + g_m r_s} \right) V_{gs} = g'_m V_{gs}$$

**The source resistance reduces the effective transconductance or transistor gain.**



# Homework16

Consider an ideal n-channel MOSFET with a width-to-length ratio of  $(W/L) = 10$ , an electron mobility of  $\mu_n = 400 \text{ cm}^2 / \text{V}\cdot\text{s}$ , an oxide thickness of  $t_{\text{ox}} = 475 \text{ \AA}$ , and a threshold voltage of  $V_T = 0.65 \text{ V}$ .

- Determine the maximum value of source resistance so that the saturation transconductance  $g_{\text{ms}}$  is reduced by no more than 20 percent from its ideal value when  $V_{\text{GS}} = 5 \text{ V}$ .
- Using the value of  $r_s$  calculated in part (a), how much is  $g_{\text{ms}}$  reduced from its ideal value when  $V_{\text{GS}} = 3 \text{ V}$ ?

