




上海交通大学
SHANGHAI JIAO TONG UNIVERSITY



Lecture 19


Transistor Amplifiers (I)

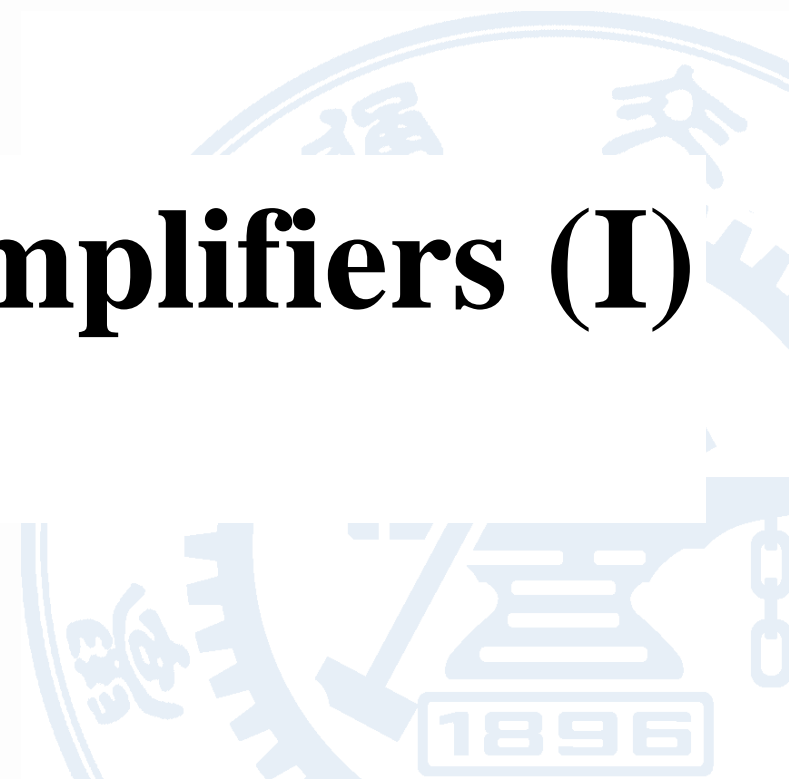



Contents:

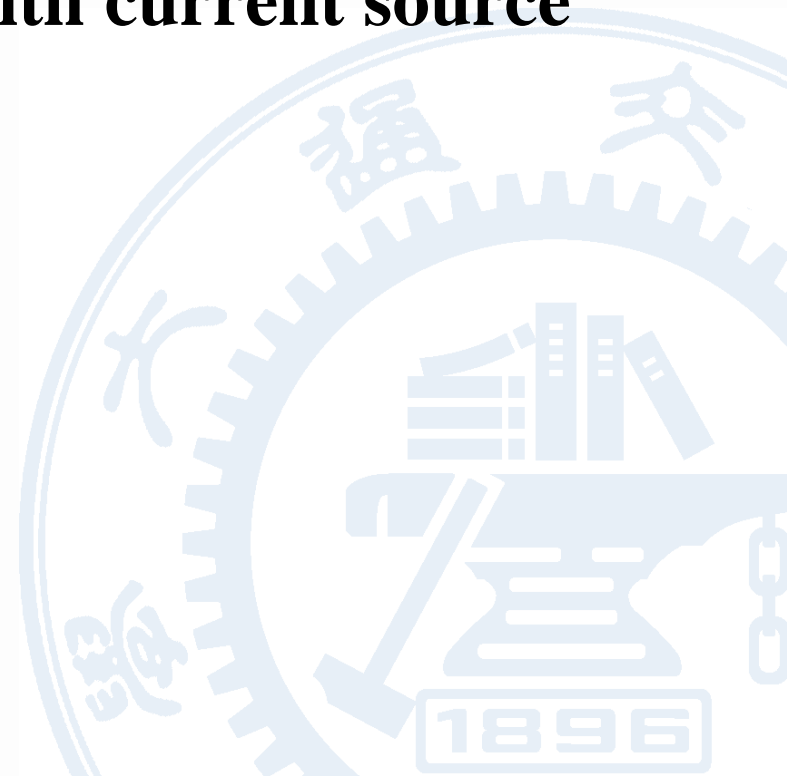
- 1. Amplifier fundamentals**
- 2. Common source amplifier**
- 3. Common source amplifier with current source supply**





Key questions


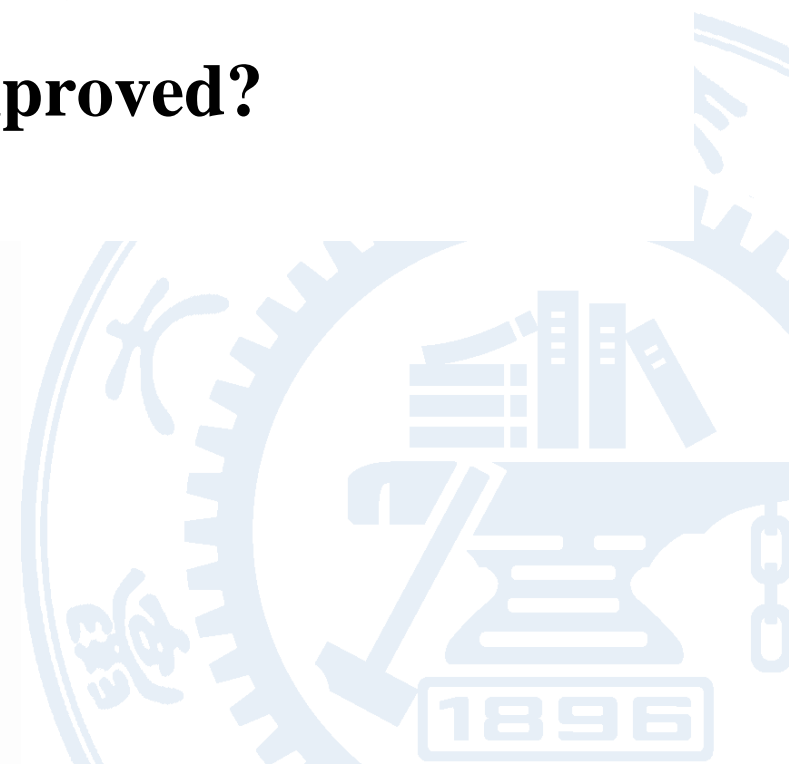
- **What are the key figures of merit of an amplifier?**
- **How can one make a voltage amplifier with a single MOSFET and a resistor?**
- **How can this amplifier be improved?**





Amplifier fundamentals

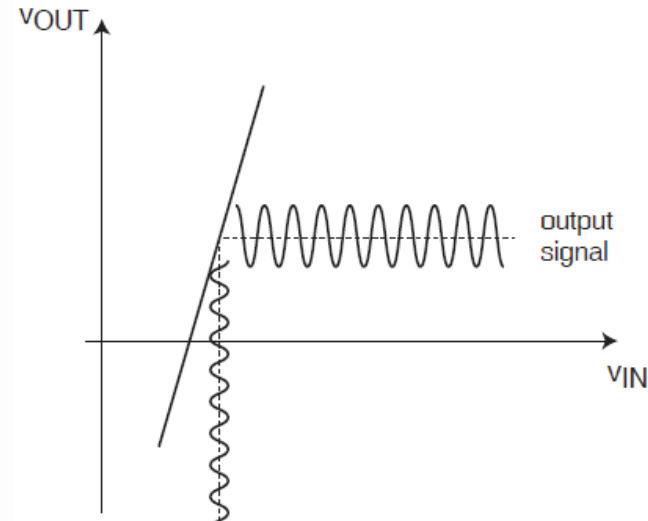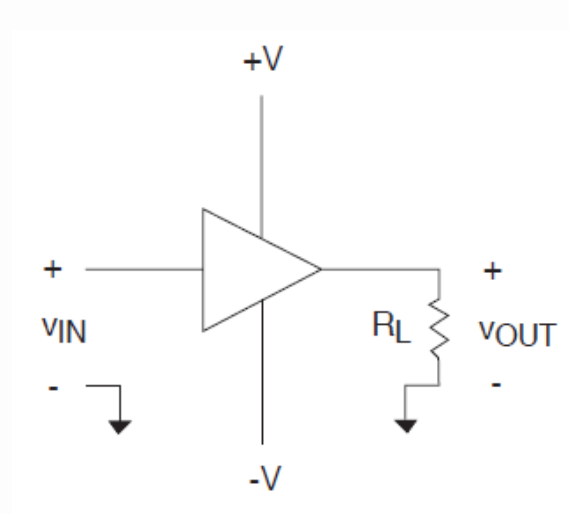◆ Goal of amplifiers: signal amplification








Features of amplifier:

- Output signal is faithful replica of input signal but amplified in magnitude.
- Active device is at the heart of amplifier. Need linear transfer characteristics for distortion not to be introduced.




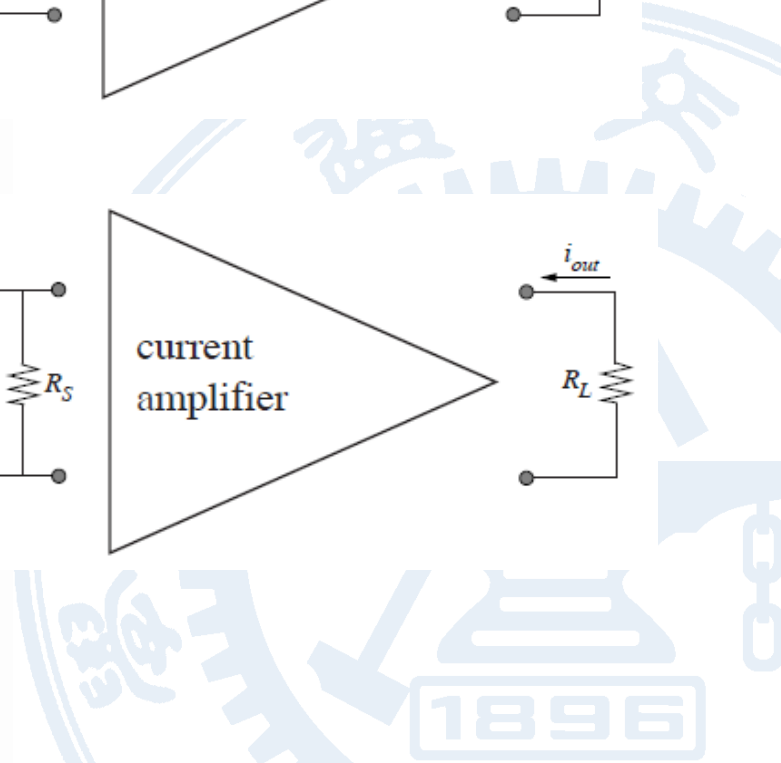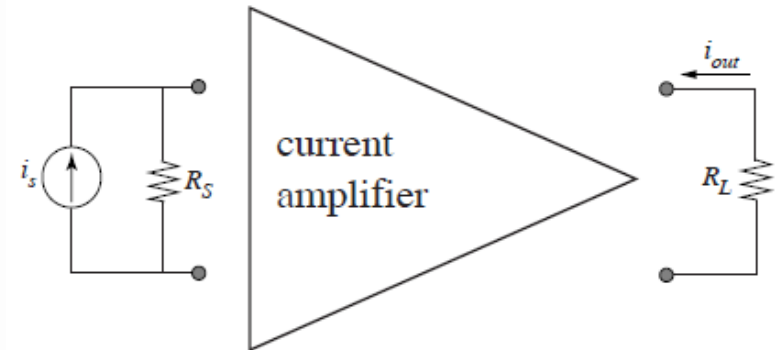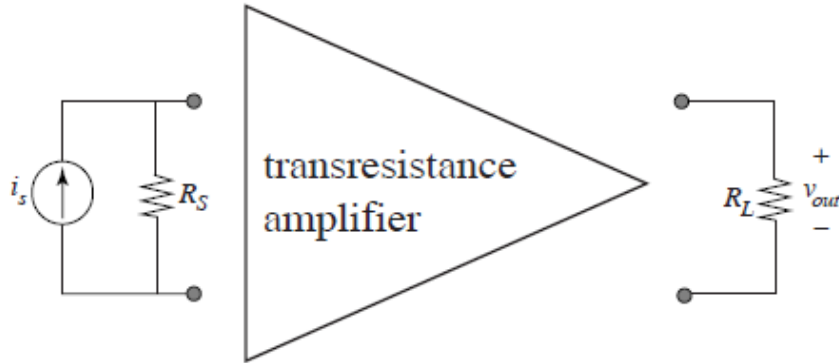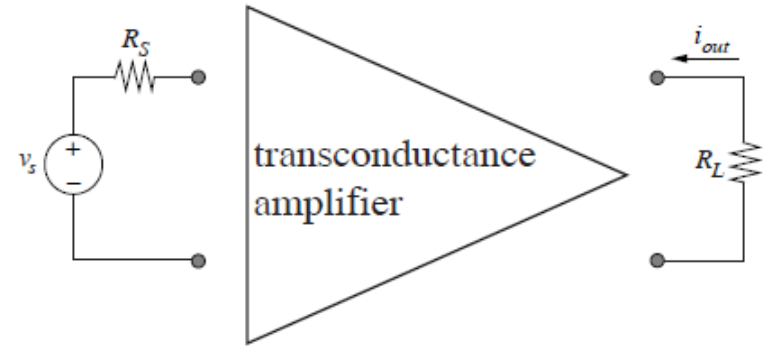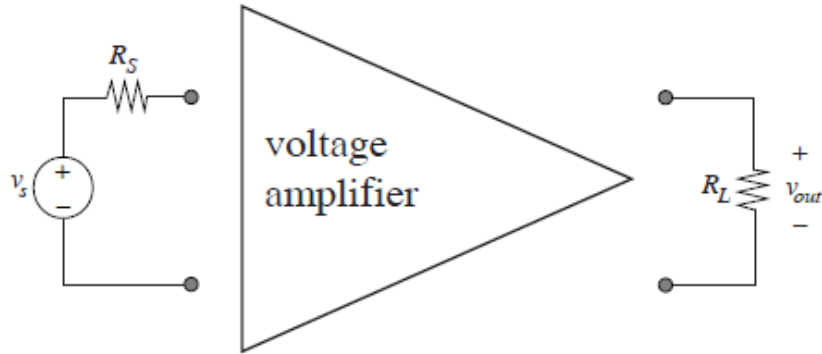Signal could be represented by current or voltage
⇒ four broad types of amplifiers:





More realistic transfer characteristics:

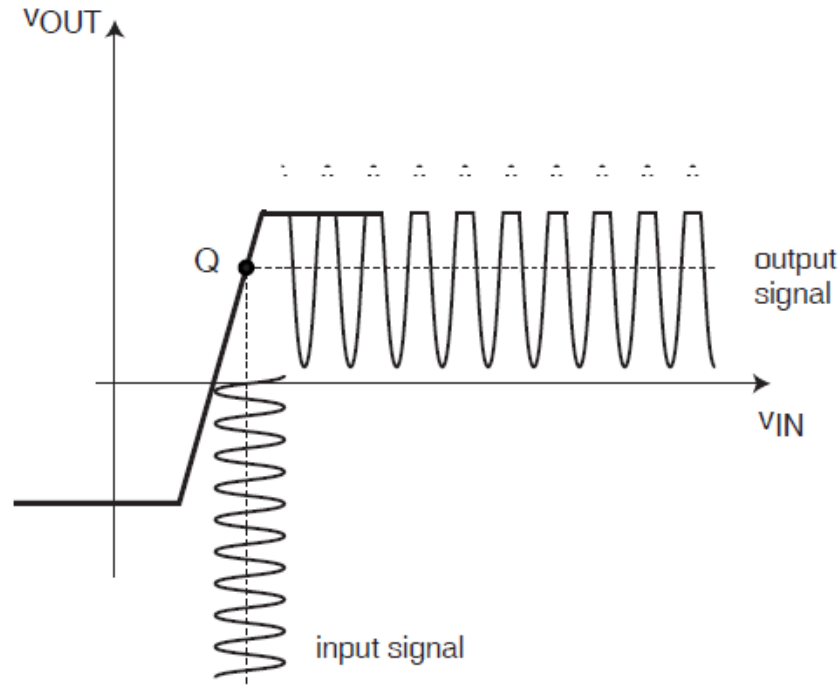


- Transfer characteristics linear over limited range of voltages: amplifier saturation.
- Amplifier saturation limits signal swing.
- Signal swing also depends on choice of bias point, Q (also called quiescent point or operating point).




Other features desired in amplifiers:

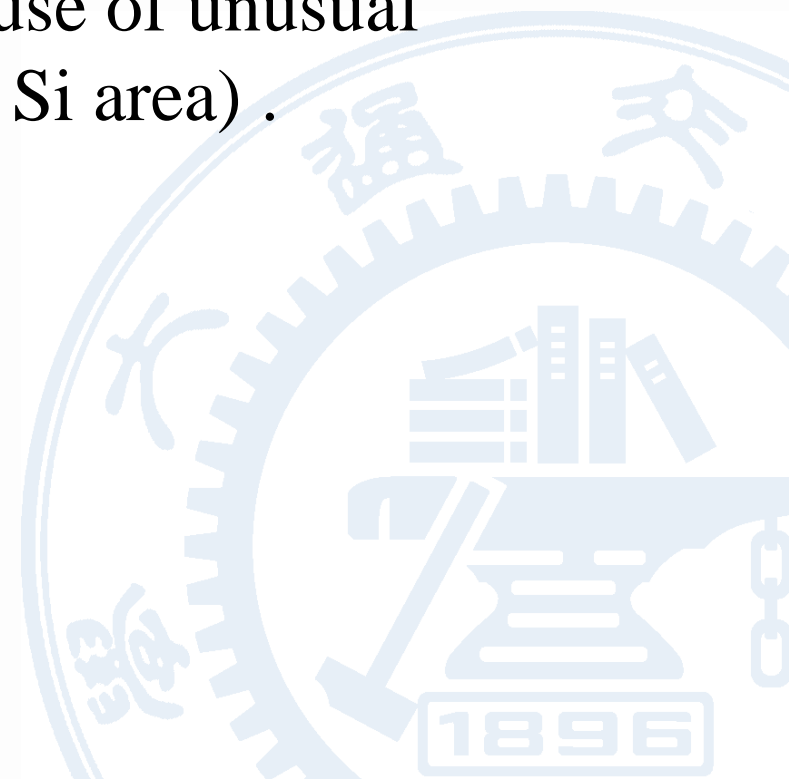- Low power consumption.
- Wide frequency response
- Robustness to process and temperature variations.
- Inexpensive: must minimize use of unusual components, must be small (in Si area).





1. Common Source Amplifier

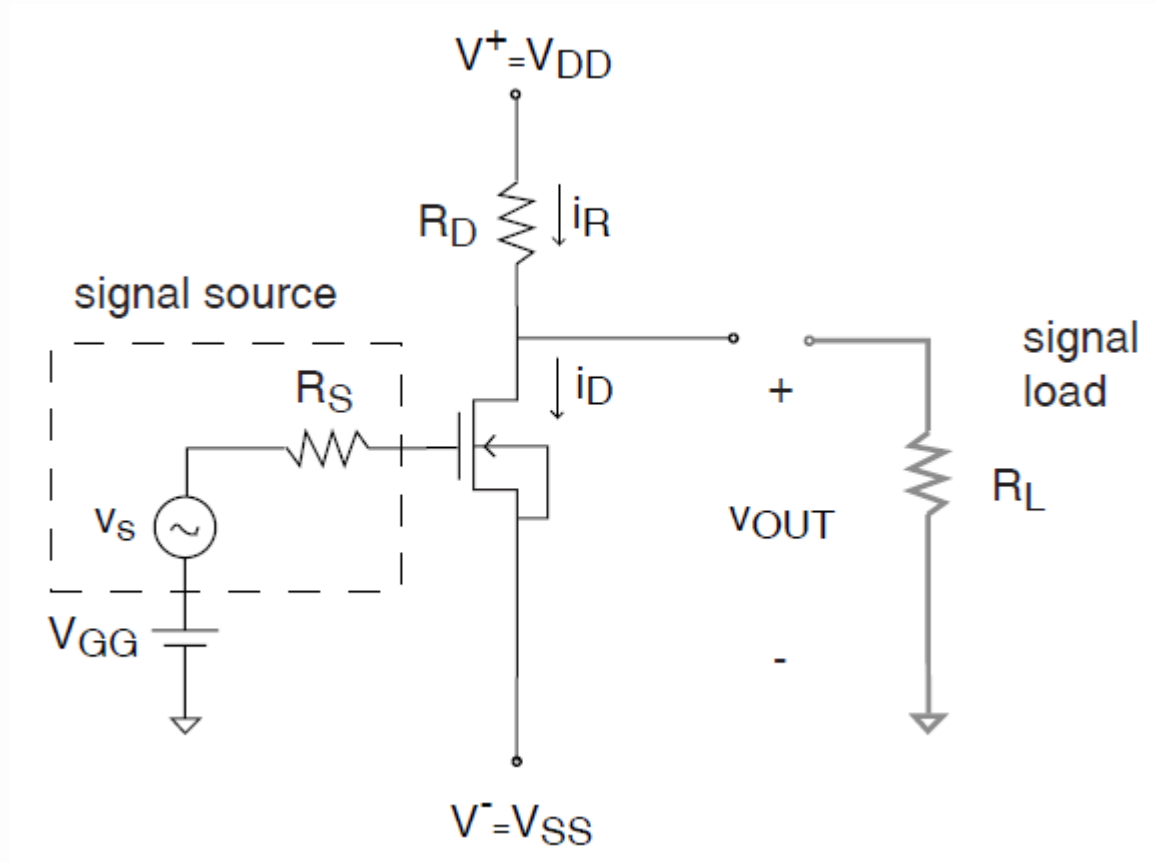

Consider it first unloaded by R_L . How does it work?






- V_{GG} , R_D and W/L of MOSFET selected to bias transistor in saturation and obtain desired output bias point (i.e. $V_{OUT}=0$)
- $v_{GS} \uparrow \Rightarrow i_D \uparrow \Rightarrow i_R \uparrow \Rightarrow v_{out} \downarrow$
- $A_v = \frac{v_{out}(t)}{v_s} < 0$;output out of phase from input, but if amplifier well designed, $|A_v| > 1$.


[watch notation: $v_{OUT}(t) = V_{OUT} + v_{out}(t)$]



Load line view of amplifier:

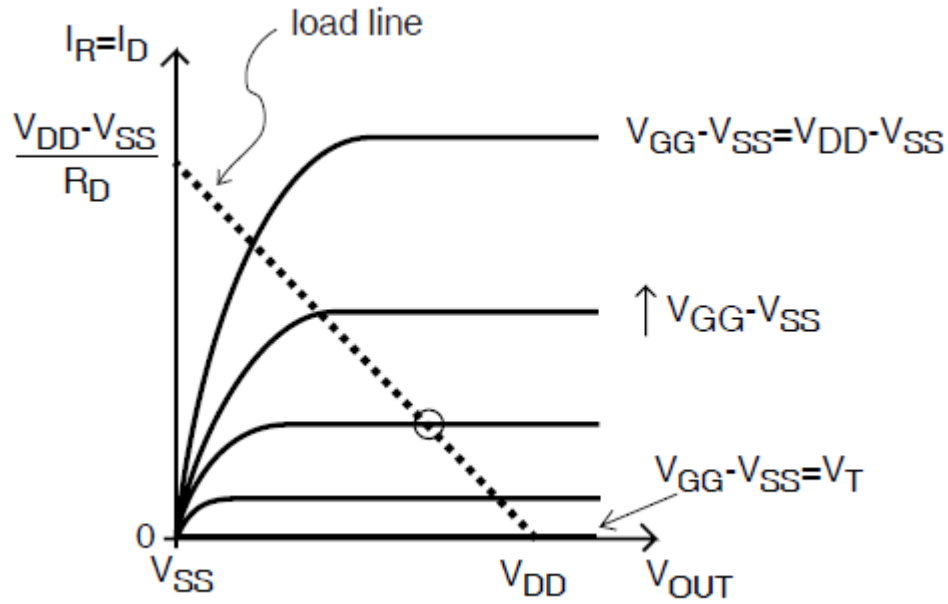

Transfer characteristics of amplifier:

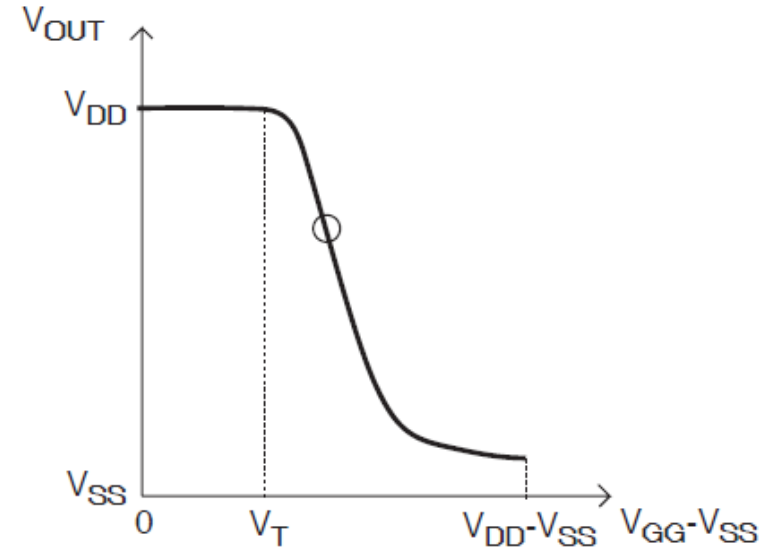

Want:

Bias point calculation;

Small signal gain;

limits to signal swing

Wide frequency response





□ Bias point: choice of V_{GG} , W/L , and R_D to keep transistor in saturation and to get proper quiescent V_{OUT} .

Assume MOSFET is in saturation:


$$I_D = \frac{W}{2L} \mu_n C_{ox} (V_{GG} - V_{SS} - V_T)^2$$

$$I_R = \frac{V_{DD} - V_{OUT}}{R_D}$$

If we select $V_{OUT} = 0$:


$$I_D = I_R = \frac{W}{2L} \mu_n C_{ox} (V_{GG} - V_{SS} - V_T)^2 = \frac{V_{DD}}{R_D}$$

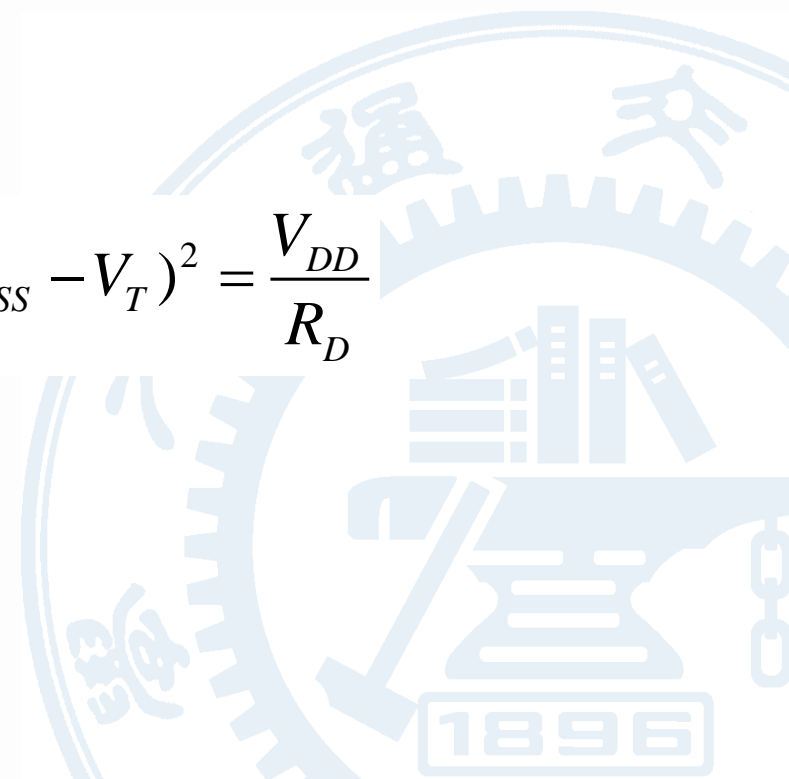Then:
$$V_{GG} = \sqrt{\frac{2V_{DD}}{R_D \frac{W}{L} \mu_n C_{ox}}} + V_{SS} + V_T$$






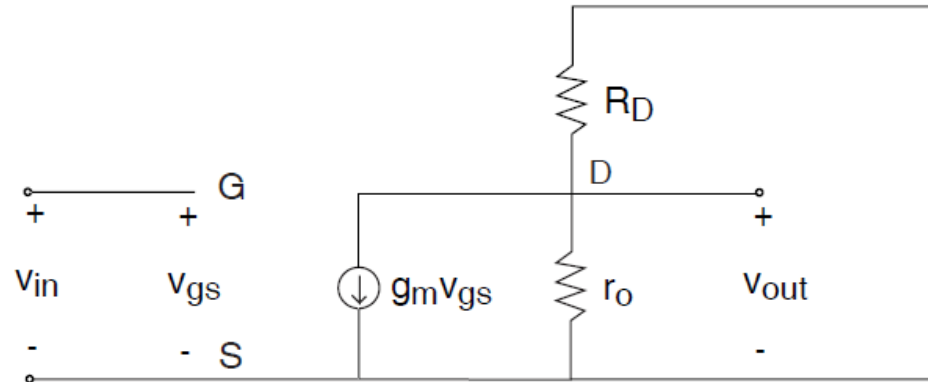□ Small signal voltage gain: draw small signal equivalent circuit model:



$$v_{out} = -g_m v_{in} (r_o // R_D)$$

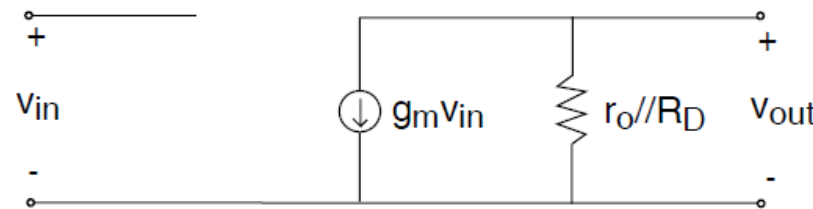

Then unloaded voltage gain:

$$A_{vo} = \frac{v_{out}}{v_{in}} = -g_m (r_o // R_D)$$



□ Signal swing:

- Upswing: limited by transistor going into cutoff:

$$v_{out,max} = V_{DD}$$


- Downswing: limited by MOSFET entering linear regime:

$$V_{DS,sat} = V_{GS} - V_T$$

$$v_{out,min} - V_{SS} = V_{GG} - V_{SS} - V_T$$


Then:

$$v_{out,min} = V_{GG} - V_T$$

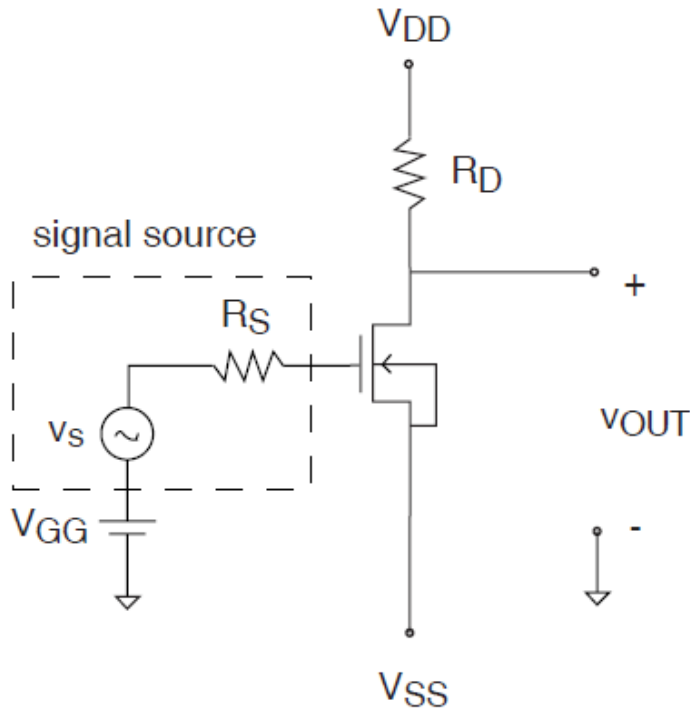



□ Effect of input/output loading:

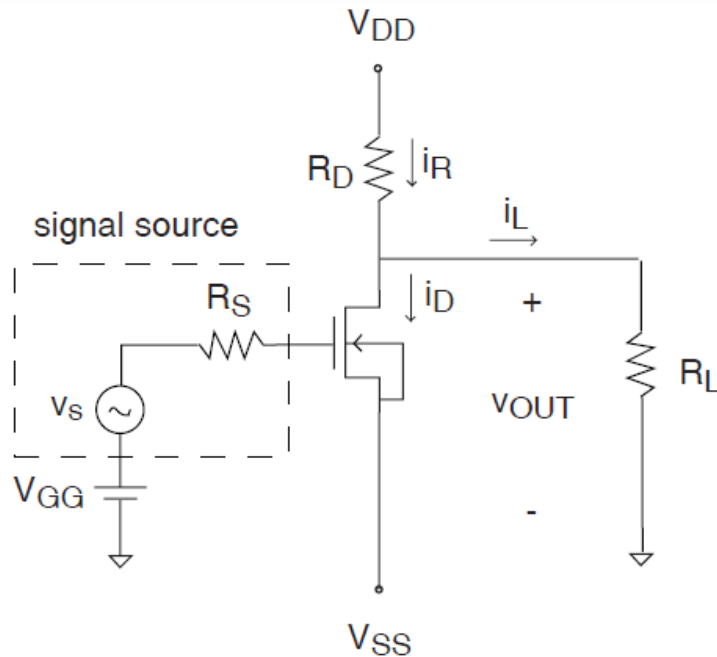

- Bias point is not affected because selected $V_{OUT} = 0$.

- Signal swing:

- Upswing limited by resistive divider:

$$v_{out,max} = V_{DD} \frac{R_L}{R_L + R_D}$$

- Downswing not affected by loading

- Voltage gain:

- input loading (R_S): no effect because gate does not draw current;

- output loading (R_L): R_L detracts from voltage gain because it draws current.


$$|A_v| = g_m (r_o // R_D // R_L) < g_m (r_o // R_D)$$



□ Generic view of loading effect on small signal operation:

Two port network view of small signal equivalent circuit model of voltage amplifier:

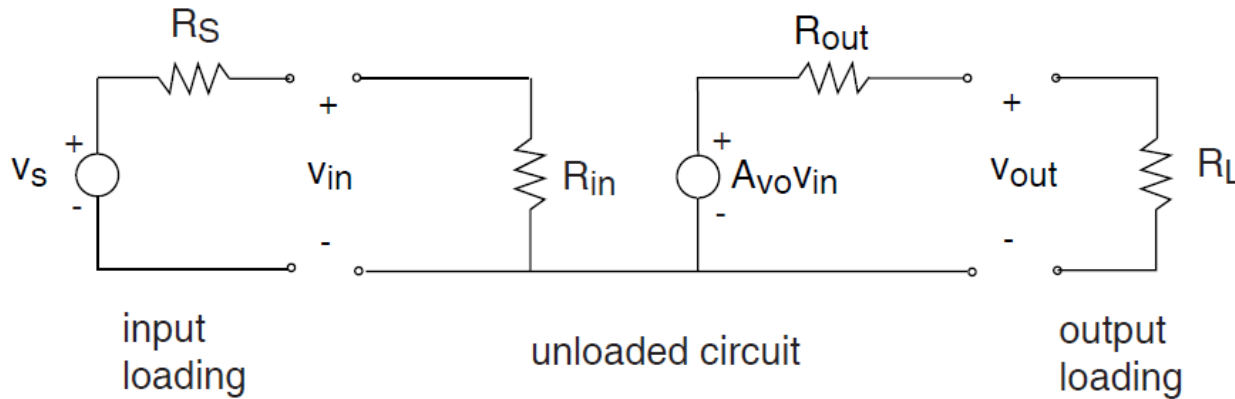R_{in} is input resistance; R_{out} is output resistance; A_{vo} is unloaded voltage gain



Voltage divider at input:
$$v_{in} = R_{in} \frac{v_s}{R_{in} + R_S}$$


Voltage divider at output:
$$v_{out} = R_L \frac{A_{vo} v_{in}}{R_{out} + R_L}$$

Loaded voltage gain:
$$A_v = \frac{v_{out}}{v_s} = \frac{R_{in}}{R_{in} + R_S} A_{vo} \frac{R_L}{R_L + R_{out}}$$



- Calculation of input resistance, R_{in} :
load amplifier with R_L ; apply test voltage (or current) at input,
measure test current (or voltage)

For common source amplifier:

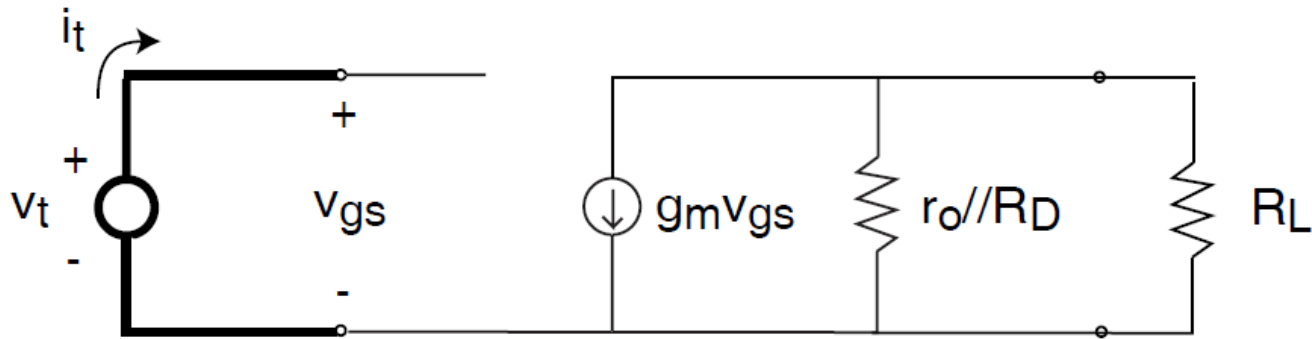


$$i_t = 0 \Rightarrow R_{in} = \frac{v_t}{i_t} = \infty$$

No effect of loading at input.



- Calculation of output resistance, R_{out} :
load amplifier at input with R_S apply test voltage (or current)
at output, measure test current (or voltage)

For common source amplifier:

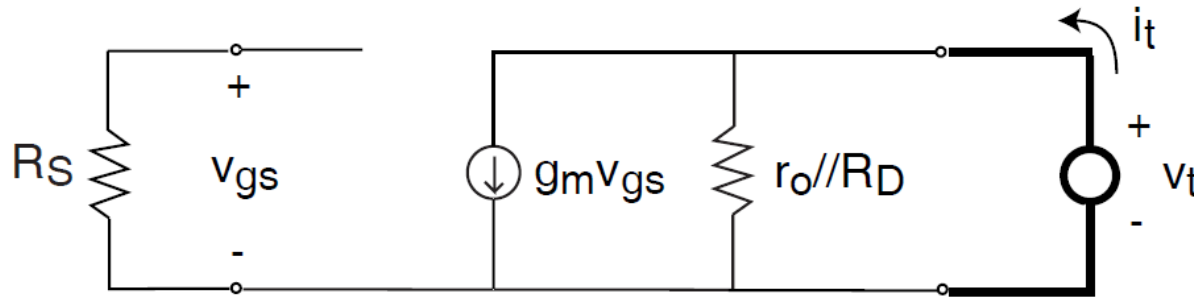


$$v_{gs} = 0 \Rightarrow g_m v_{gs} = 0 \Rightarrow v_t = i_t (r_o // R_D)$$

$$R_{out} = \frac{v_t}{i_t} = r_o // R_D$$



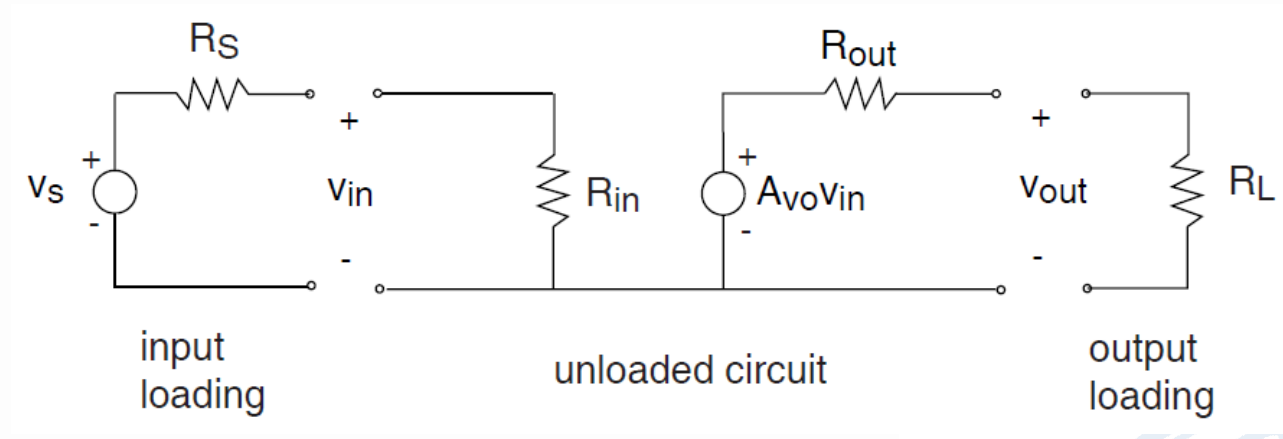
Two port network view of common source amplifier:



$$A_v = \frac{v_{out}}{v_s}$$

$$= \frac{R_{in}}{R_{in} + R_S} A_{vo} \frac{R_L}{R_L + R_{out}} = -g_m (r_o // R_D) \frac{R_L}{R_L + r_o // R_D}$$

$$A_v = -g_m (r_o // R_D // R_L)$$

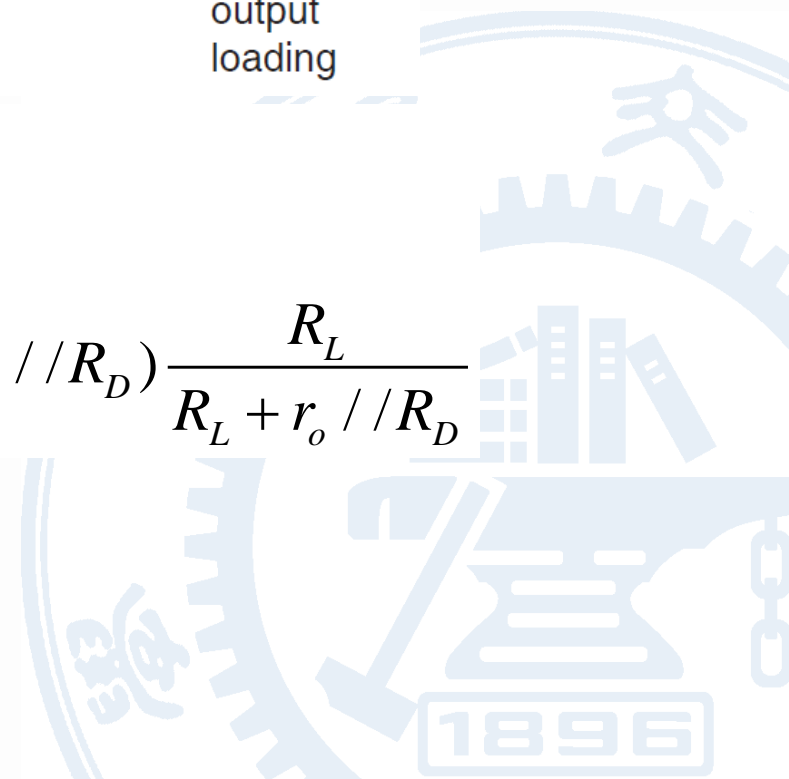



□ Design issues of common source amplifier (unloaded):

Examine bias dependence:

$$|A_{vo}| = g_m (r_o // R_D) \approx g_m R_D$$

Rewrite A_{vo} in the following way:

$$|A_{vo}| = g_m R_D = \sqrt{2 \frac{W}{L} \mu_n C_{ox} I_D} \frac{V_{DD}}{I_D} \propto \frac{V_{DD}}{\sqrt{I_D}}$$

Then, to get high $|A_{vo}|$:

$$\Rightarrow V_{DD} \uparrow$$

$$\Rightarrow I_D \downarrow$$

$$\text{Both approaches imply } \Rightarrow R_D = \frac{V_{DD}}{I_D} \uparrow$$


Consequences of high R_D :

large R_D consumes a lot of Si real state

large R_D eventually compromises frequency response





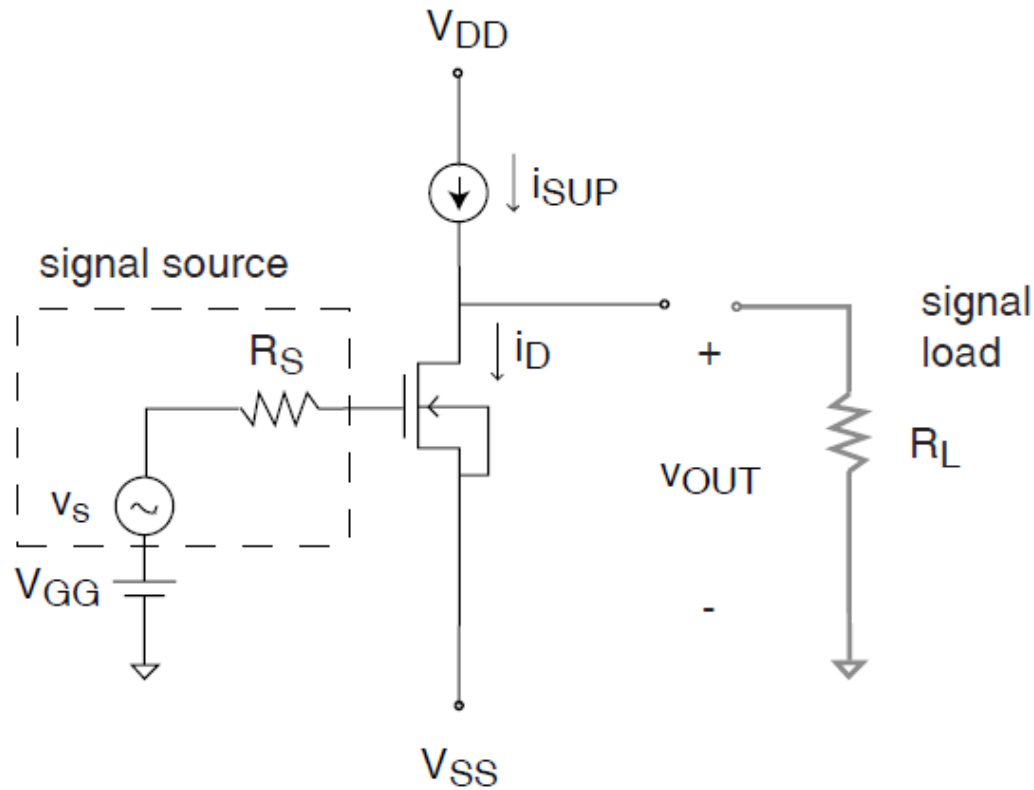2. Common source amplifier with current source supply





Loadline view:

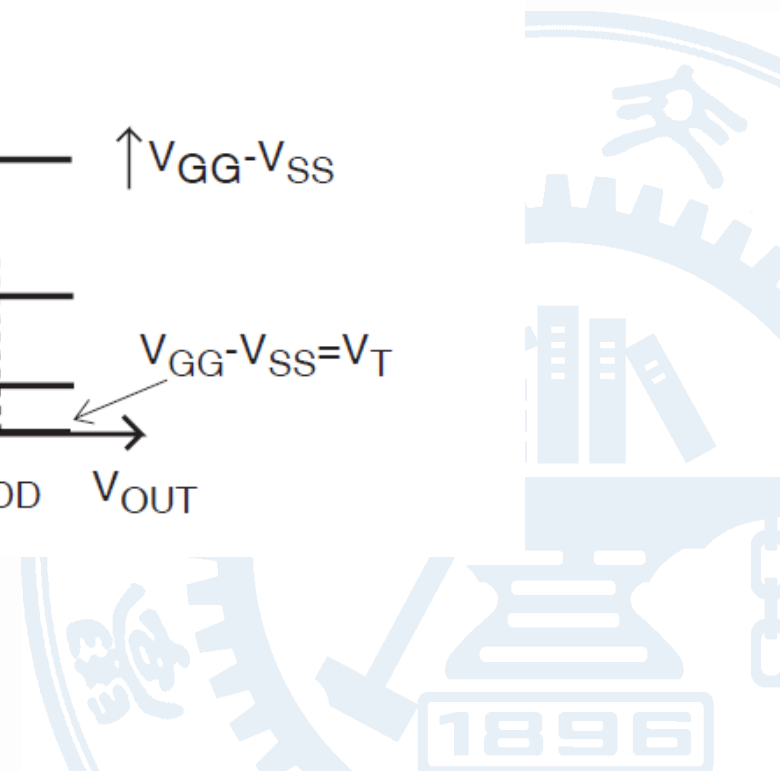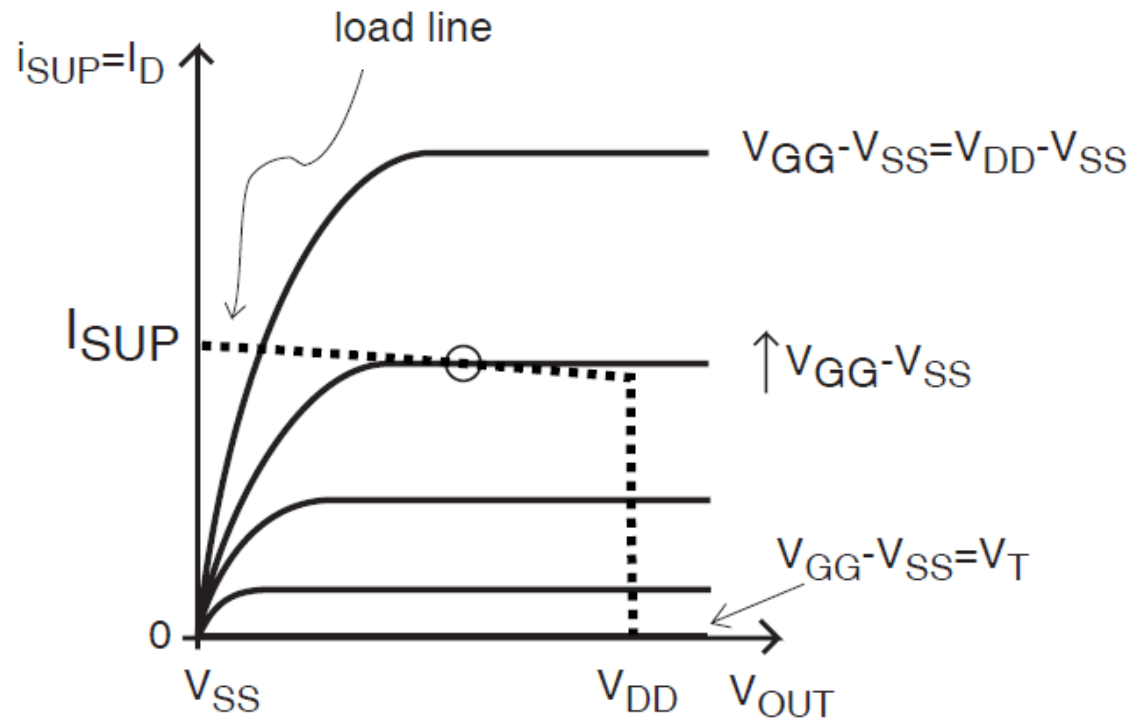




Current source characterized by high output resistance: r_{oc}
 Then, unloaded voltage gain of common source stage:

$$|A_{vo}| = g_m (r_o // r_{oc})$$

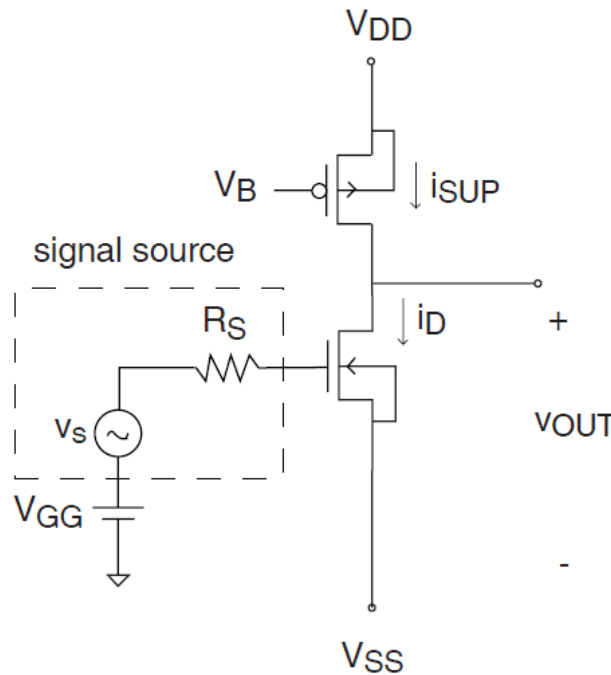significantly higher than amplifier with resistive supply.
 Can implement current source supply by means of p channel MOSFET:



Upswing limited by PMOS entering linear regime

$$V_{out,max} = V_B - V_{Tp}$$



• Relationship between circuit figures of merit and device parameters

Remember:

$$g_m = \sqrt{2 \frac{W}{L} \mu_n C_{ox} I_D}$$

$$r_o \approx \frac{1}{\lambda_n I_D} \propto \frac{L}{I_D}$$

Then

Device * Parameters	Circuit Parameters		
	$ A_{vo} $	R_{in}	R_{out}
	$g_m(r_o // r_{oc})$	∞	$r_o // r_{oc}$
$I_{SUP} \uparrow$	\downarrow	-	\downarrow
$W \uparrow$	\uparrow	-	-
$\mu_n C_{ox} \uparrow$	\uparrow	-	-
$L \uparrow$	\uparrow	-	\uparrow

CS amp with current supply source is voltage amplifier


(R_{in} high and $|A_v|$ high), but R_{out} high too

\Rightarrow voltage gain degraded if $R_L \ll r_o // r_{oc}$




Common-source amplifier is acceptable voltage amplifier
(want high R_{in} , high A_{vo} , low R_{out}):

This is the problem

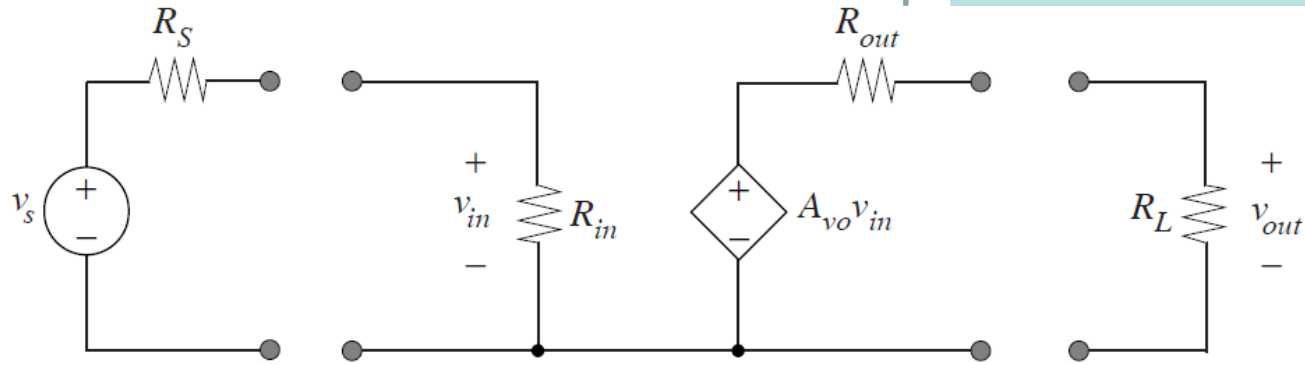

... but **excellent transconductance amplifier**

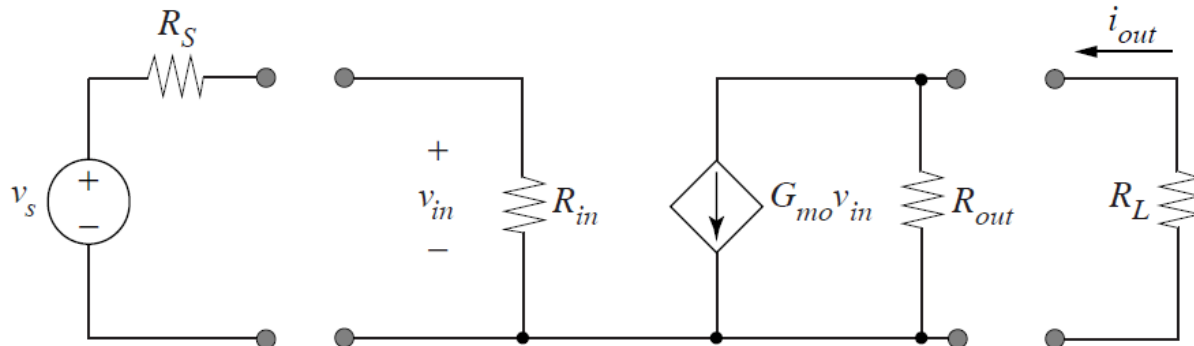
(want high R_{in} , high G_{mo} , high R_{out}): $G_{mo} = g_m$






Common-source amplifier does not work as transresistance amplifier (want low R_{in} , high R_{mo} , low R_{out}):

Key problem

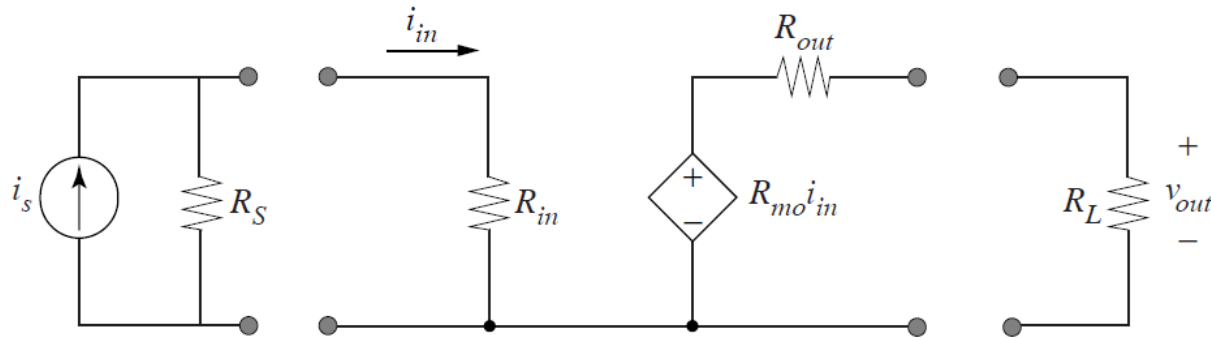

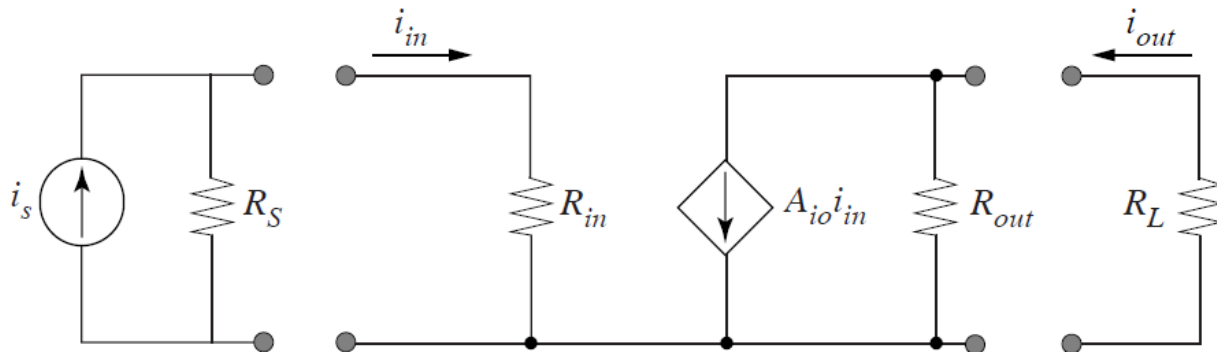not as current amplifier (want low R_{in} , high A_{io} , high R_{out}):



Need new amplifier configurations.



Key conclusions

- Figures of merit of an amplifier:
 - gain
 - signal swing
 - power consumption
 - frequency response
 - robustness to process and temperature variations
- Common source amplifier with resistive supply: tradeoff between gain and cost and frequency response.
- Tradeoff resolved by using common source amplifier with current source supply.
- Two port network computation of voltage gain, input resistance and output resistance of amplifier.